




Impedance Matching

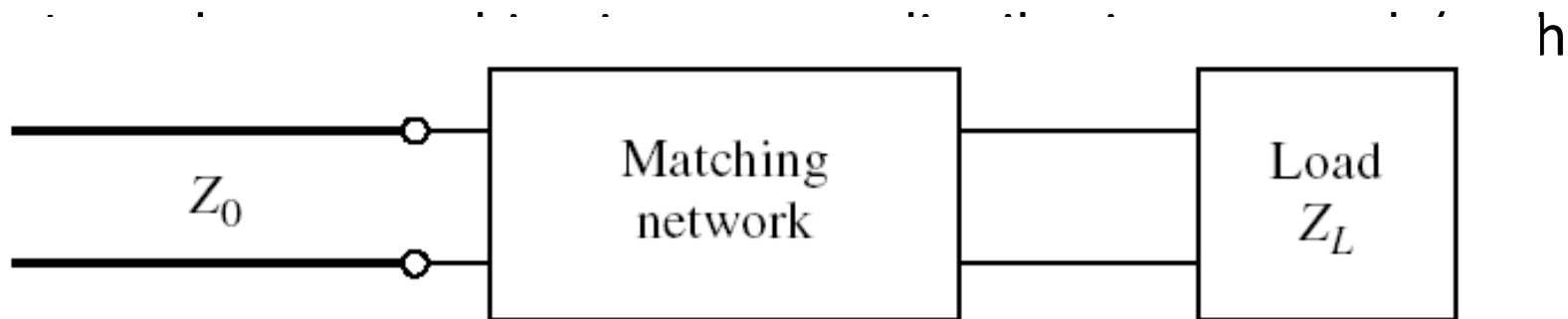A. Nassiri -ANL



- Impedance matching is important for the following reasons:
 - Maximum power is delivered when the load is matched to the line (assuming the generator is matched), and power loss in is minimized.
 - Impedance matching sensitive receiver components (antenna, low-noise amplifier, etc.) improves the signal-to-noise ratio of the system.







- Factors that may be important in the selection of a particular matching network include the following:
 - **Complexity:**
 - A simpler matching network is usually cheaper, more reliable, and less lossy than a more complex design.
 - **Bandwidth:**
 - Narrow or broadband.
 - **Implementation:**
 - According to the technology used the matching network can be decided on.
 - **Adjustability:**
 - Required if dealing with variable load.



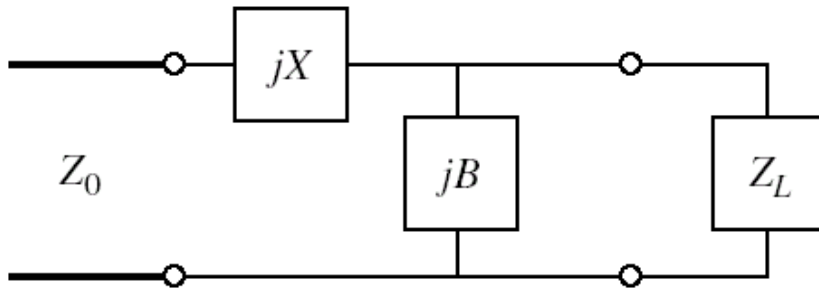
Matching with lumped elements (L-Networks)



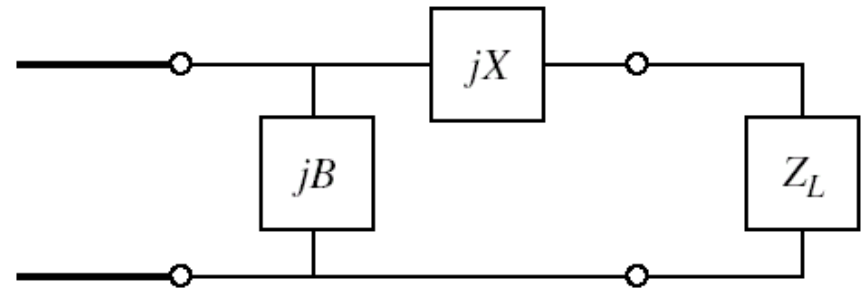Network for z_L inside the $1 + jx$ circle



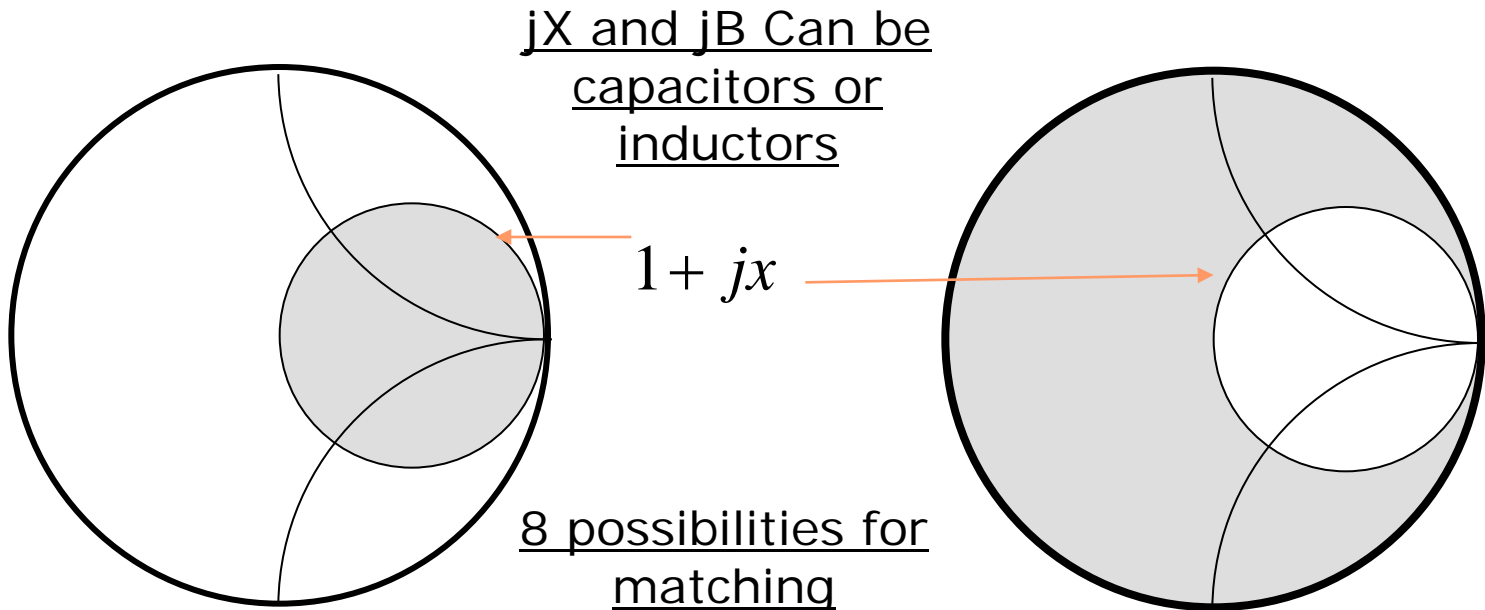Network for z_L outside the $1 + jx$ circle





Analytic Solutions

$$Z_L = R_L + jX_L \quad z_L = \frac{Z_L}{Z_o}$$


$$Z_o = Z_L // \left(\frac{1}{jB} \right) + jX$$

$$Z_o = jX + \frac{1}{jB + 1/(R_L + jX_L)}$$

$$Z_o = jX + \frac{R_L + jX_L}{jB(R_L + jX_L) + 1} = jX + \frac{R_L + jX_L}{(1 - BX_L) + jBR_L}$$

$$Z_o = \frac{jX((1 - BX_L) + jBR_L) + R_L + jX_L}{(1 - BX_L) + jBR_L}$$
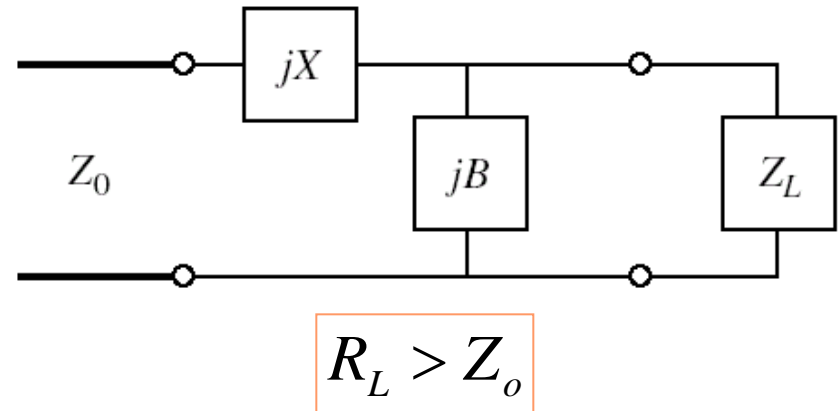
$$Z_o = \frac{(R_L - XBR_L) + j(X_L + X(1 - BX_L))}{(1 - BX_L) + jBR_L}$$





$$\Re_{LH} = \Re_{RH}$$

$$Z_o(1 - BX_L) = (R_L - XBR_L) \longrightarrow B(XR_L - X_LZ_o) = R_L - Z_o$$

$$\Im_{LH} = \Im_{RH}$$

$$BR_LZ_o = X_L + X(1 - BX_L) \longrightarrow X(1 - BX_L) = BZ_oR_L - X_L$$

Solving the 2nd order equation

$$B = \frac{X_L \pm \sqrt{R_L/Z_o} \sqrt{R_L^2 + X_L^2 - Z_oR_L}}{R_L^2 + X_L^2}$$

But $R_L > Z_o$

$$B(XR_L - X_LZ_o) = R_L - Z_o \longrightarrow X = \frac{1}{B} + \frac{X_LZ_o}{R_L} - \frac{Z_o}{BR_L}$$



Analytic Solutions

$$Z_L = R_L + jX_L$$

$$\frac{1}{Z_o} = jB + \frac{1}{R_L + j(X + X_L)}$$

$$\frac{1}{Z_o} = \frac{jB(R_L + j(X + X_L)) + 1}{R_L + j(X + X_L)}$$

$$R_L + j(X + X_L) = Z_o \left((1 - B(X + X_L)) + jBR_L \right)$$

$$\Re_{LH} = \Re_{RH}$$


$$\Im_{LH} = \Im_{RH}$$

$$BZ_o(X + X_L) = Z_o - R_L$$

$$(X + X_L) = BZ_o R_L$$

$$X = \pm \sqrt{R_L(Z_o - R_L)} - X_L$$
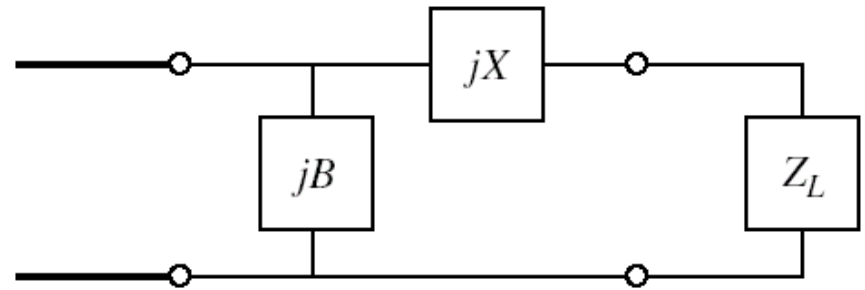
$$B = \pm \frac{\sqrt{(Z_o - R_L)/R_L}}{Z_o}$$



$$R_L < Z_o$$



Smith Chart Solutions

Example


Design an L-section matching network to match a series RC load with an impedance $Z_L = 200 - j100 \Omega$, to a 100Ω , at a frequency of 500 MHz.

Solution

$$Z_L = 200 - j100 \Omega$$


$$R_L > Z_0$$

$$z_L = 2 - j1 \Omega$$

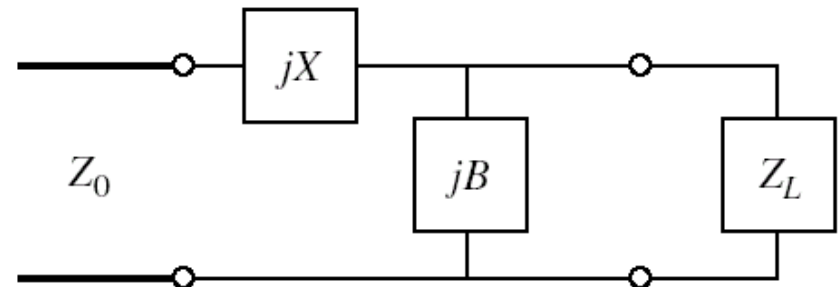

1st Step


$$z_L = 2 - j1\Omega$$

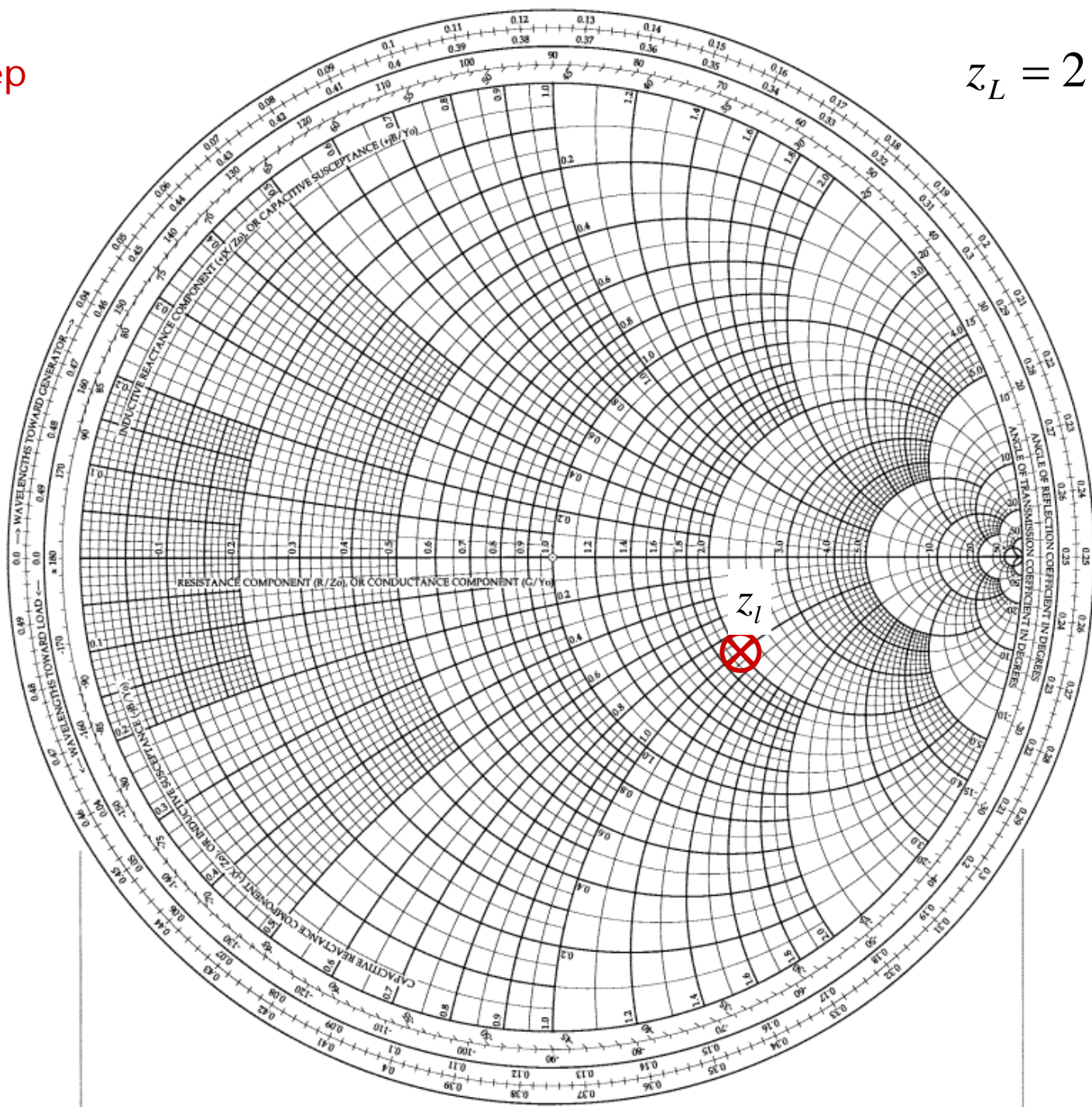

2st Step


$$y_l = 0.4 + j0.2$$

OP = OQ

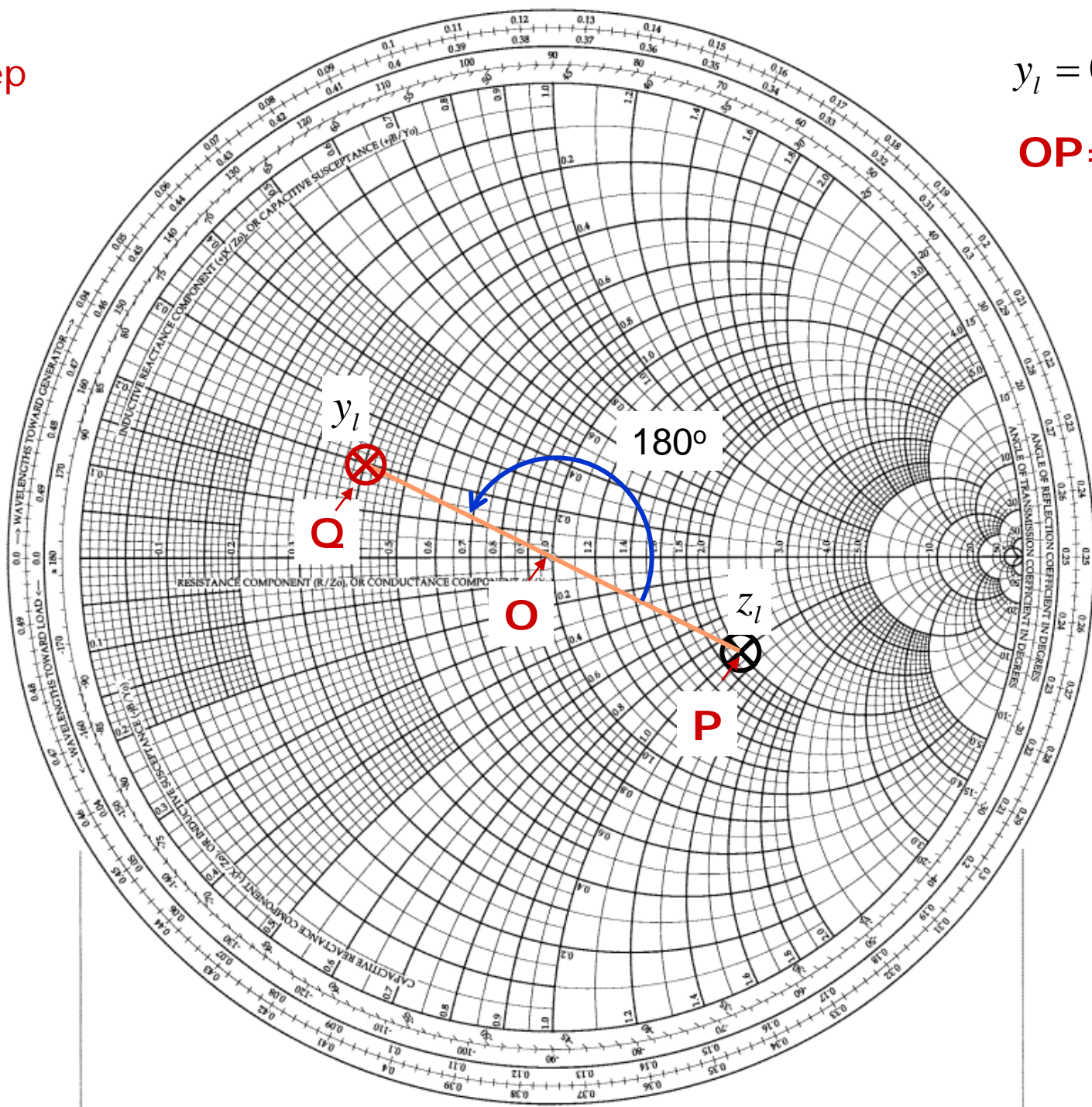


3rd Step

$$y_l = 0.4 + j0.2$$

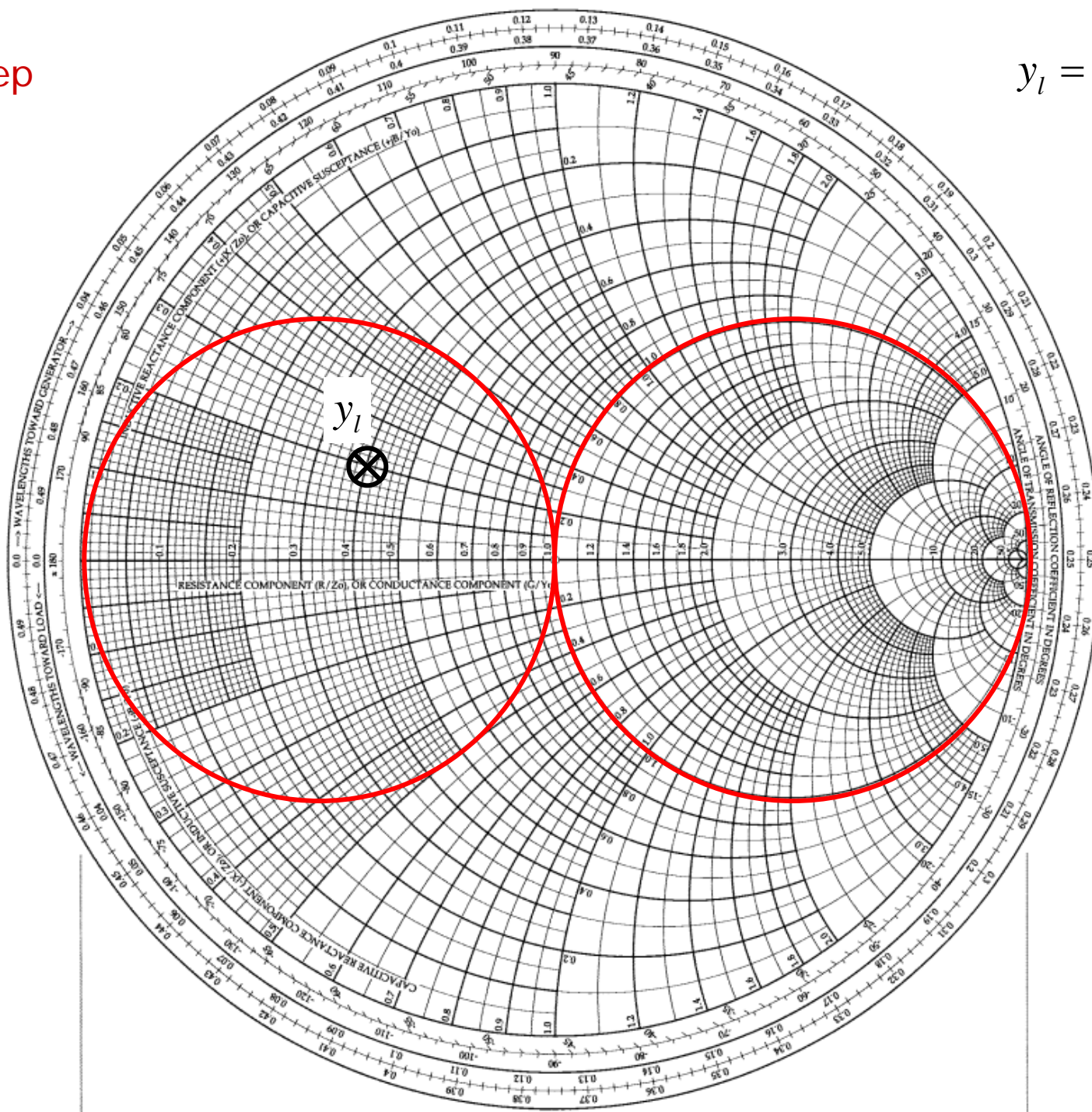

4th Step

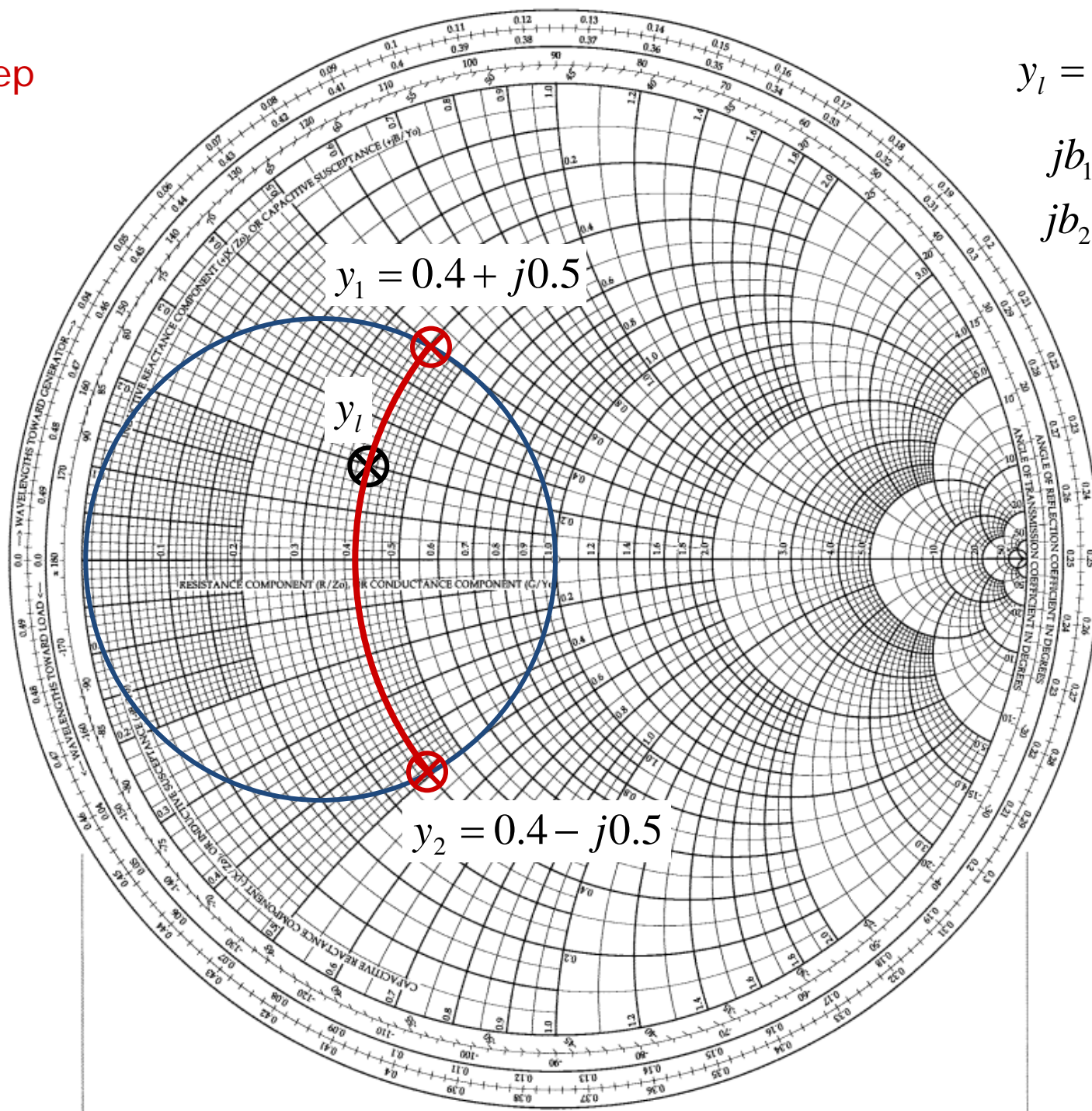


$$y_I = 0.4 + j0.2$$

$$jb_1 = j0.3$$

$$jb_2 = -j0.7$$

4th Step

Sol. 1

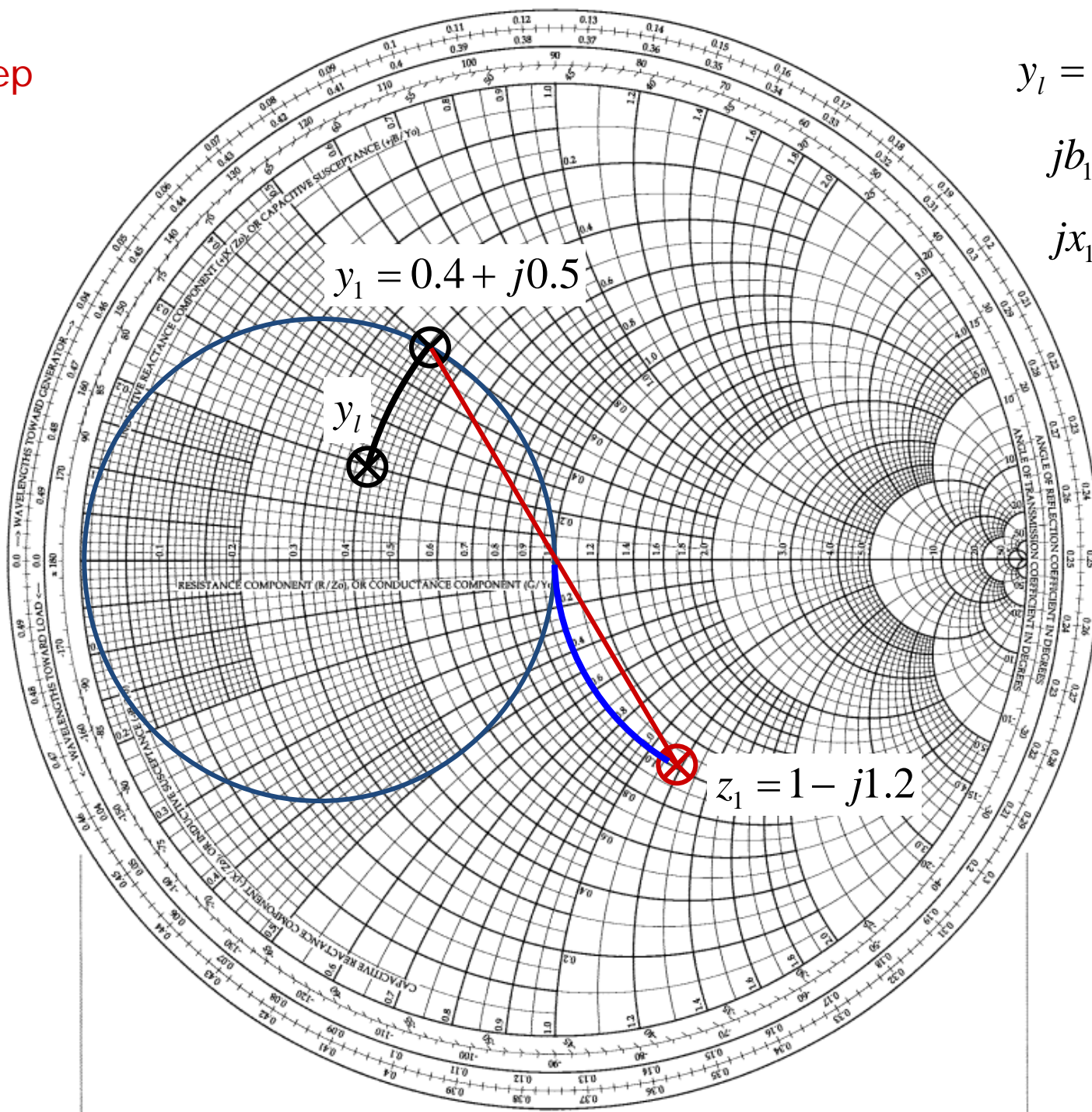


$$y_i = 0.4 + j0.2$$

$$jb_1 = j0.3$$

$$jx_1 = +j1.2$$

4th Step

Sol. 2

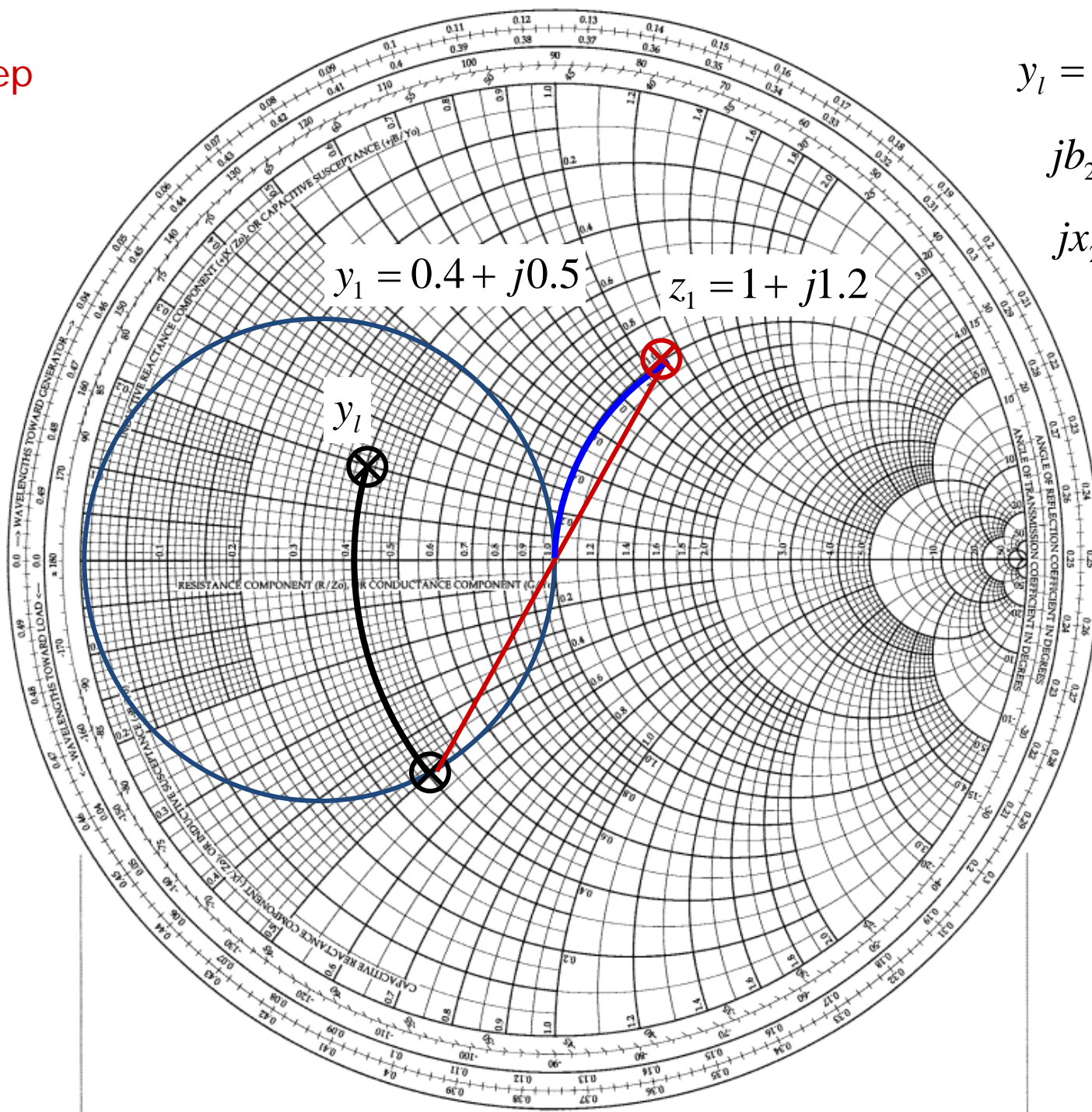

$$y_I = 0.4 + j0.2$$

$$j b_2 = -j0.7$$

$$j x_2 = -j1.2$$

$$y_1 = 0.4 + j0.5$$


$$z_1 = 1 + j1.2$$



Example

$$jb_1 = j0.3$$

$$jx_1 = +j1.2$$

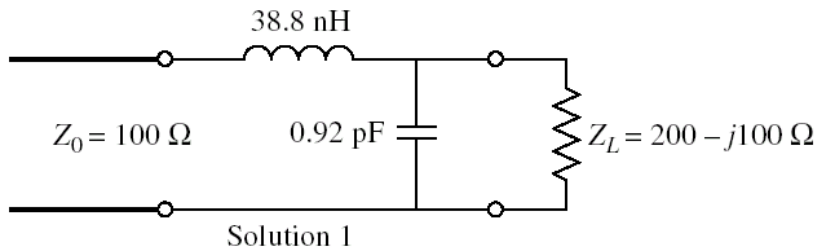

$$jB = jb \times \frac{1}{Z_o} = j\omega C$$


$$C = \frac{b}{\omega Z_o} = \frac{0.3}{2\pi(500 \times 10^6)100} = 0.955 \text{ pF}$$

$$jX = jx \times Z_o = j\omega L$$

$$L = \frac{xZ_o}{\omega} = \frac{1.2 \times 100}{2\pi(500 \times 10^6)} = 38.2 \text{ nH}$$

$$jb_2 = -j0.7$$

$$jx_2 = -j1.2$$

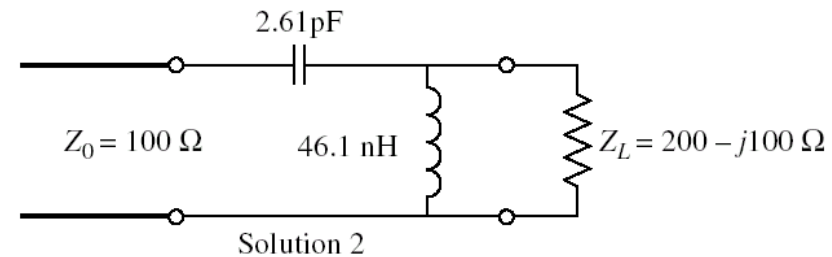


$$jB = jb \times \frac{1}{Z_o} = \frac{-j}{\omega L}$$

$$L = \frac{-Z_o}{\omega b} = \frac{-100}{2\pi(500 \times 10^6)(-0.7)} = 45.5 \text{ nH}$$

$$jX = jx \times Z_o = \frac{-j}{\omega C}$$
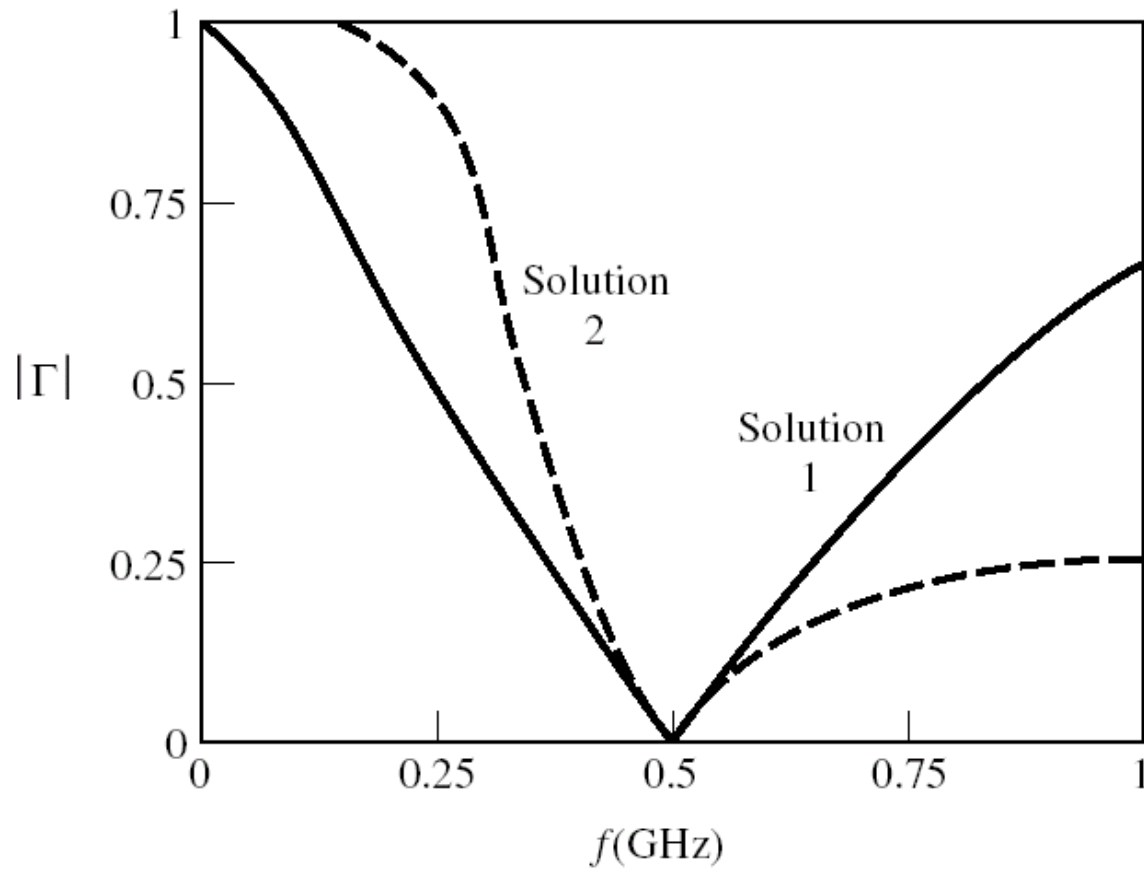
$$C = \frac{-1}{\omega x Z_o} = \frac{-1}{2\pi(500 \times 10^6) \times (-1.2) \times 100} = 2.65 \text{ pF}$$






The Quarter Wave Transformer

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l}$$

$$Z_{in} = Z_1 \frac{\frac{Z_L}{\tan \beta l} + jZ_1}{\frac{Z_1}{\tan \beta l} + jZ_L} = Z_1 \frac{\frac{Z_L}{\tan \frac{\pi}{2}} + jZ_1}{\frac{Z_1}{\tan \frac{\pi}{2}} + jZ_L} = \frac{Z_L}{Z_1} = Z_o$$

$$Z_1 = \sqrt{Z_o Z_L}$$

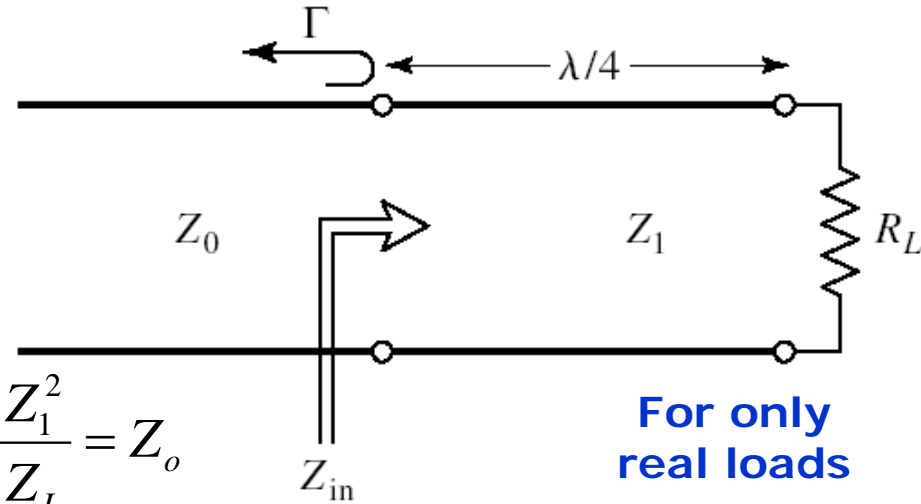

Need to drive the mismatch versus frequency?

Let $t = \tan \beta l = \tan \theta$ at $f = f_o$ $\theta = \frac{\pi}{2}$ $Z_{in} = Z_1 \frac{Z_L + jZ_1 t}{Z_1 + jZ_L t}$

$$\Gamma = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{Z_1 \left(\frac{Z_L + jZ_1 t}{Z_1 + jZ_L t} \right) - Z_o}{Z_1 \left(\frac{Z_L + jZ_1 t}{Z_1 + jZ_L t} \right) + Z_o} = \frac{Z_1(Z_L + jZ_1 t) - Z_o(Z_1 + jZ_L t)}{Z_1(Z_L + jZ_1 t) + Z_o(Z_1 + jZ_L t)}$$



$$\Gamma = \frac{Z_1(Z_L - Z_o) + jt(Z_1^2 - Z_o Z_L)}{Z_1(Z_L + Z_o) + jt(Z_1^2 + Z_o Z_L)} \quad \& \quad Z_1^2 = Z_o Z_L$$

$$\Gamma = \frac{\cancel{Z_1}(Z_L - Z_o)}{\cancel{Z_1}(Z_L + Z_o) + j2t\cancel{Z_1}} \quad \Gamma = \frac{Z_L - Z_o}{Z_L + Z_o + j2t\sqrt{Z_o Z_L}} \rightarrow |\Gamma|$$

$$|\Gamma| = \frac{|Z_L - Z_o|}{\left((Z_L + Z_o)^2 + 4t^2 Z_o Z_L\right)^{1/2}} = \frac{1}{\left(\frac{(Z_L + Z_o)^2}{(Z_L - Z_o)^2} + \left(4t^2 Z_o Z_L / (Z_L - Z_o)^2\right)\right)^{1/2}}$$

$$\frac{(Z_L + Z_o)^2}{(Z_L - Z_o)^2} = 1 + \frac{4Z_o Z_L}{(Z_L - Z_o)^2}$$

$$|\Gamma| = \frac{1}{\left(1 + 4Z_o Z_L / (Z_L - Z_o)^2 + \left(4t^2 Z_o Z_L / (Z_L - Z_o)^2\right)\right)^{1/2}} = \frac{1}{\left(1 + \left(4Z_o Z_L / (Z_L - Z_o)^2\right) \sec^2 \theta\right)^{1/2}}$$

$$1 + t^2 = 1 + \tan^2 \theta = \sec^2 \theta \quad \left(4Z_o Z_L / (Z_L - Z_o)^2\right) \sec^2 \theta > 1$$



The Quarter Wave Transformer

If we are operating close to f_o $l \approx \frac{\lambda_o}{4}$ $\theta \approx \frac{\pi}{2}$ $\sec^2 \theta \gg 1$

$$|\Gamma| \approx \frac{|Z_L - Z_o|}{2\sqrt{Z_o Z_L}} |\cos \theta|$$

$$\Delta\theta = 2\left(\frac{\pi}{2} - \theta_m\right)$$


$$\frac{1}{\Gamma_m^2} = 1 + \left(\frac{2\sqrt{Z_o Z_L}}{Z_L - Z_o} \sec \theta_m\right)^2$$

$$\cos \theta_m = \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_o Z_L}}{|Z_L - Z_o|}$$

$$\theta = \beta l = \frac{2\pi f}{v_p} \frac{v_p}{4f_o} = \frac{\pi f}{2f_o}$$

$$f_m = \frac{2\theta_m f_o}{\pi}$$


Quarter Wavelength at f_o

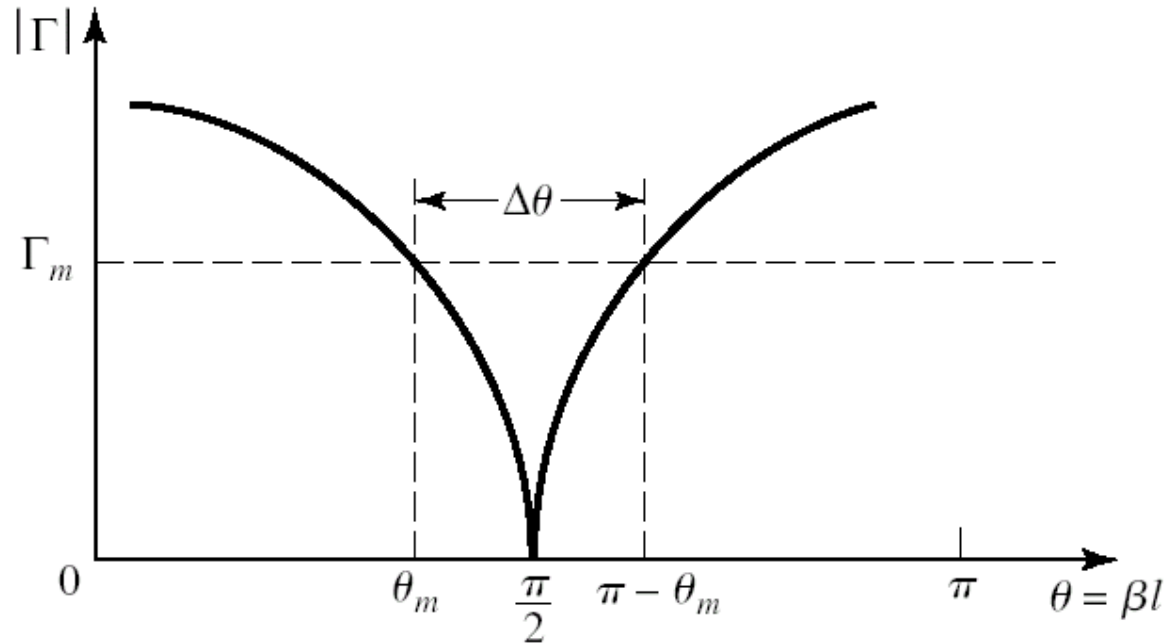

Γ_m = Maximum reflection coefficient magnitude that can be tolerated



$$\frac{\Delta f}{f_o} = \frac{2(f_o - f_m)}{f_o} = 2 - \frac{2f_m}{f_o} = 2 - \frac{4\theta_m}{\pi} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_o Z_L}}{|Z_L - Z_o|} \right]$$

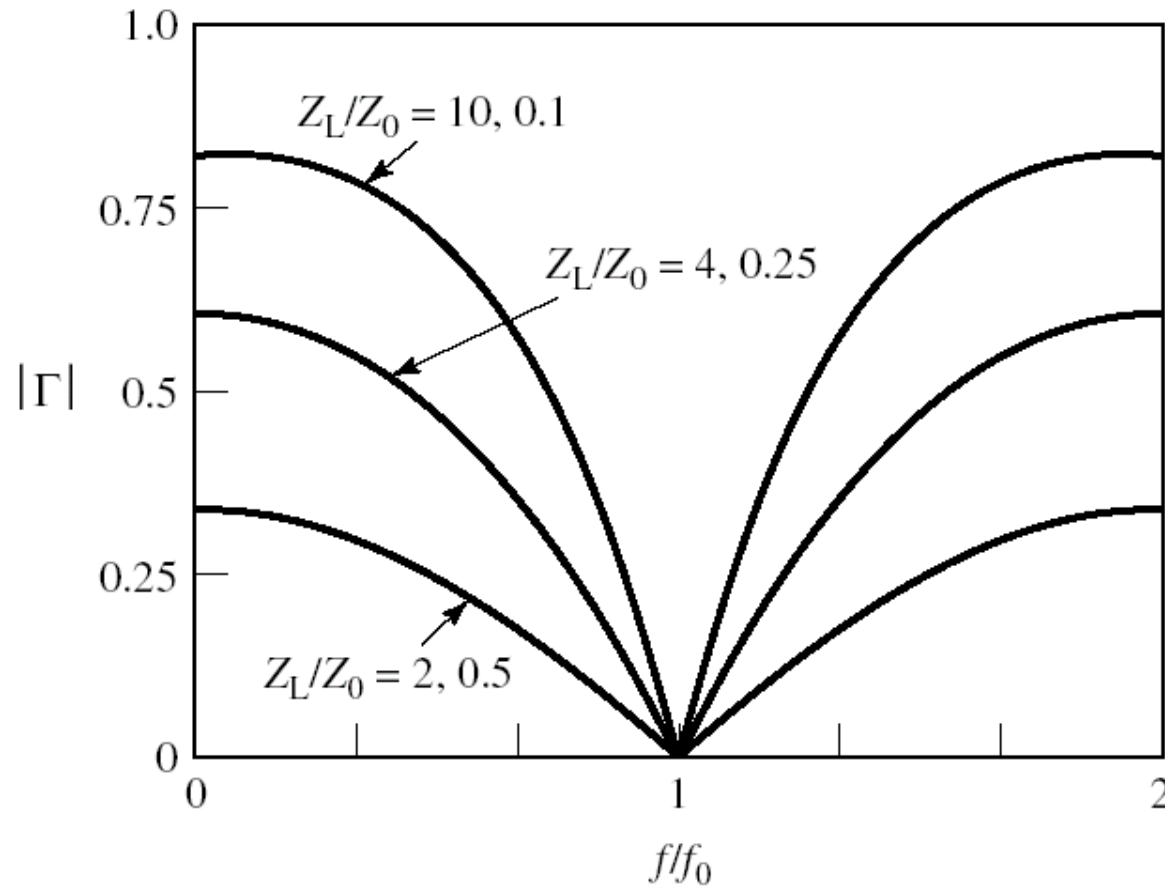



Design a single-section quarter-wave matching transformer to match a 10Ω load to a 50Ω line, at $f_o = 3 \text{ GHz}$. Determine the percent bandwidth for which the $\text{SWR} \leq 1.5$.

Solution

$$Z_1 = \sqrt{Z_o Z_L} = \sqrt{(50)(10)} = 22.36 \Omega$$


$$\text{Length } \lambda/4 \quad @ 3 \text{ GHz} \quad \Gamma_m = \frac{\text{SWR} - 1}{\text{SWR} + 1} = \frac{1.5 - 1}{1.5 + 1} = 0.2$$

$$\frac{\Delta f}{f_o} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_o Z_L}}{|Z_L - Z_o|} \right]$$

$$\frac{\Delta f}{f_o} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{0.2}{\sqrt{1 - (0.2)^2}} \frac{2\sqrt{(50)(10)}}{|10 - 50|} \right] = 0.29, \text{ or } 29\%$$

- Single-Section Transformer

$\Gamma?$

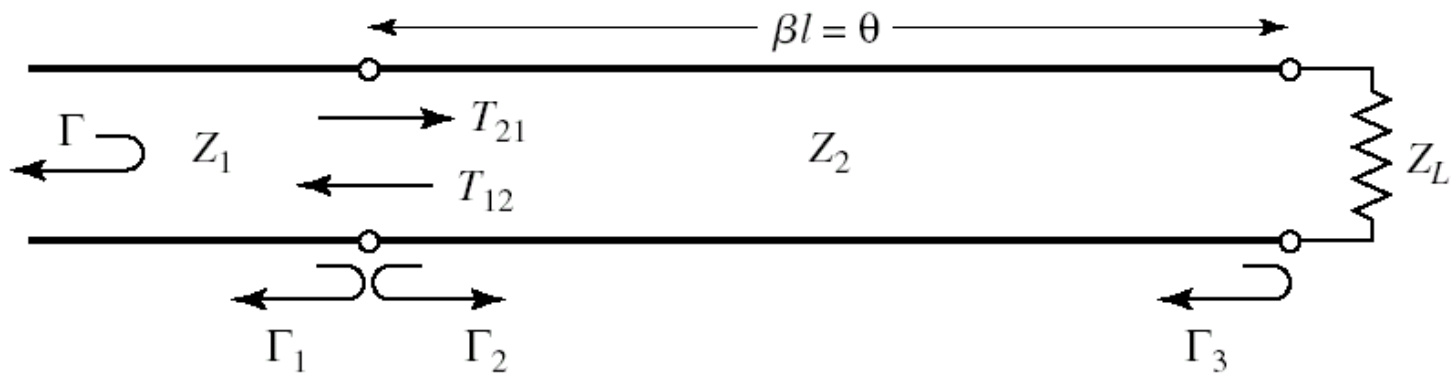


$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$\Gamma_2 = -\Gamma_1$$

$$T_{21} = 1 + \Gamma_1 = \frac{2Z_2}{Z_1 + Z_2}$$

$$T_{12} = 1 + \Gamma_2 = \frac{2Z_1}{Z_1 + Z_2}$$
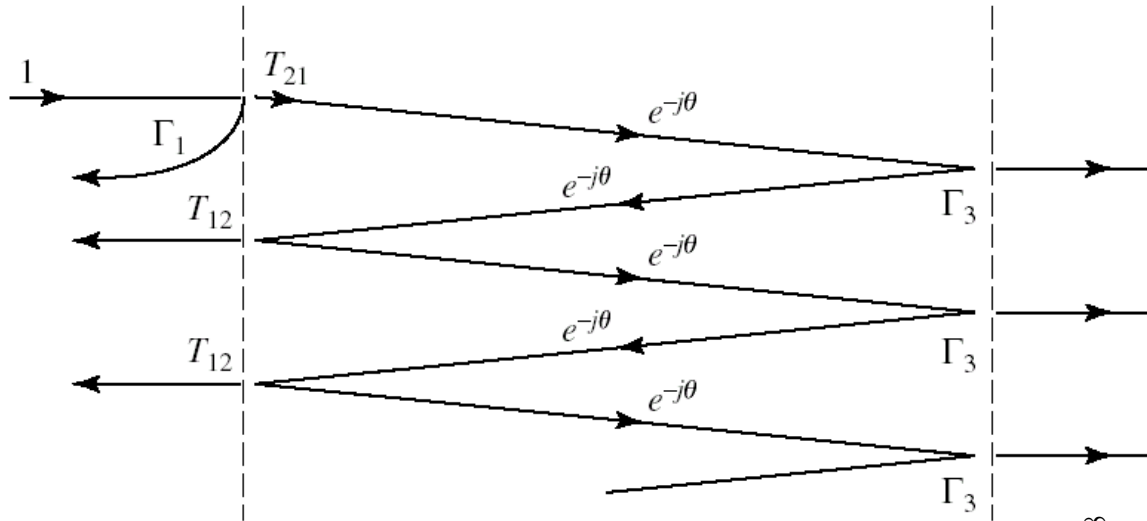
$$\Gamma_3 = \frac{Z_L - Z_2}{Z_L + Z_2}$$



$$\Gamma = \Gamma_1 + T_{12}T_{21}\Gamma_3e^{-2j\theta} + T_{12}T_{21}\Gamma_3\Gamma_2e^{-4j\theta} + \dots = \Gamma_1 + T_{12}T_{21}\Gamma_3e^{-2j\theta} \sum_{n=0}^{\infty} \Gamma_2^n \Gamma_3^n e^{-2jn\theta}$$

$$\sum_{n=0}^{\infty} x^n = \frac{1}{1-x} \quad \text{for } |x| < 1$$

$$\Gamma = \Gamma_1 + \frac{T_{12}T_{21}\Gamma_3e^{-2j\theta}}{1 - \Gamma_2\Gamma_3e^{-2j\theta}}$$

$$\begin{aligned} \Gamma_2 &= -\Gamma_1 \\ T_{21} &= 1 + \Gamma_1 = \frac{2Z_2}{Z_1 + Z_2} \\ T_{12} &= 1 + \Gamma_2 = \frac{2Z_1}{Z_1 + Z_2} \end{aligned}$$


$$\Gamma = \Gamma_1 + \frac{(1 + \Gamma_1)(1 - \Gamma_1)\Gamma_3e^{-2j\theta}}{1 + \Gamma_1\Gamma_3e^{-2j\theta}} = \Gamma_1 + \frac{(1 - \Gamma_1^2)\Gamma_3e^{-2j\theta}}{1 + \Gamma_1\Gamma_3e^{-2j\theta}} = \frac{\cancel{\Gamma_1 + \Gamma_1^2\Gamma_3e^{-2j\theta}} + (1 - \cancel{\Gamma_1^2})\Gamma_3e^{-2j\theta}}{1 + \Gamma_1\Gamma_3e^{-2j\theta}}$$



$$\Gamma = \frac{\Gamma_1 + \Gamma_3 e^{-2j\theta}}{1 + \Gamma_1 \Gamma_3 e^{-2j\theta}}$$

If the discontinuities between the impedances Z_1 , Z_2 , and Z_2 , Z_L are small, then $|\Gamma_1 \Gamma_3| \ll 1$.
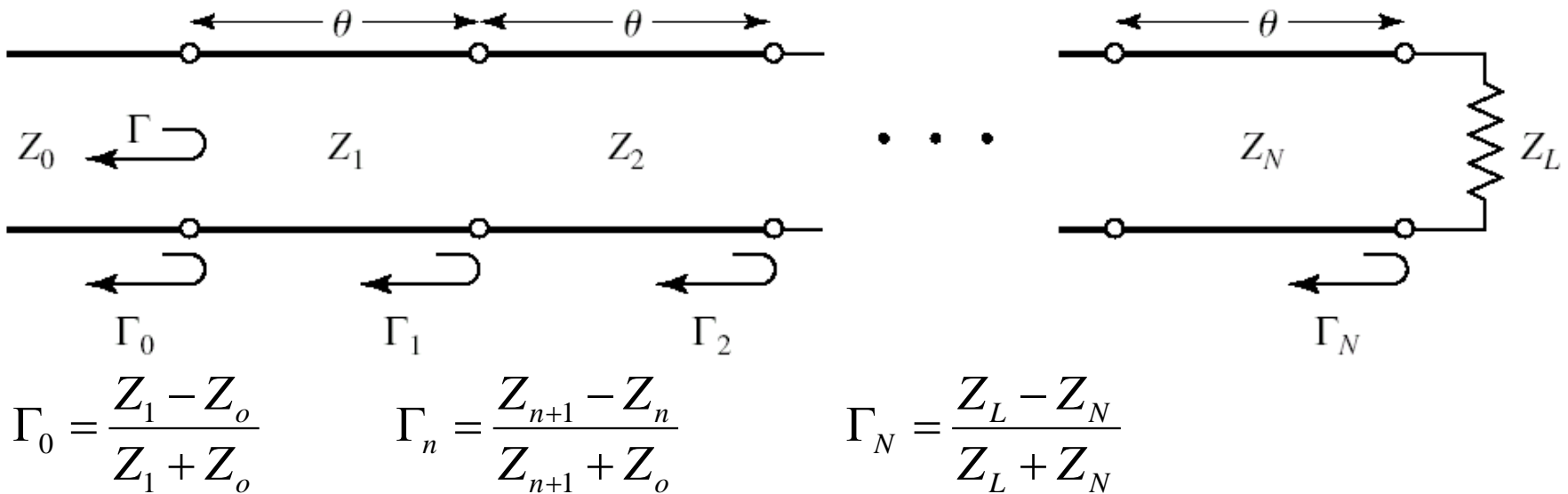
$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-2j\theta}$$



$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-2j\theta}$$

$$\Gamma = \Gamma(\theta) \cong \Gamma_0 + \Gamma_1 e^{-2j\theta} + \Gamma_2 e^{-4j\theta} + \dots + \Gamma_{N-2} e^{-2j(N-2)\theta} + \Gamma_{N-1} e^{-2j(N-1)\theta} + \Gamma_N e^{-2jN\theta}$$

Assume that the transformer is symmetrical

$$\Gamma_0 = \Gamma_N \quad \Gamma_1 = \Gamma_{N-1} \quad \Gamma_2 = \Gamma_{N-2} \quad \text{etc.}$$

$$\Gamma(\theta) = \Gamma_0 + \Gamma_1 e^{-2j\theta} + \Gamma_2 e^{-4j\theta} + \dots + \Gamma_2 e^{-2j(N-2)\theta} + \Gamma_1 e^{-2j(N-1)\theta} + \Gamma_0 e^{-2jN\theta}$$

$$\Gamma(\theta) = \Gamma_0 (1 + e^{-2jN\theta}) + \Gamma_1 (e^{-2j\theta} + e^{-2j(N-1)\theta}) + \Gamma_2 (e^{-4j\theta} + e^{-2j(N-2)\theta}) + \dots$$



$$\Gamma(\theta) = e^{-jN\theta} \left[\Gamma_0 (e^{jN\theta} + e^{-jN\theta}) + \Gamma_1 (e^{j(N-2)\theta} + e^{-j(N-2)\theta}) + \Gamma_2 (e^{j(N-4)\theta} + e^{-j(N-4)\theta}) + \dots \right]$$

$$\Gamma(\theta) = 2e^{-jN\theta} \left[\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots + \frac{1}{2} \Gamma_{N/2} \right]$$

For N even

$$\Gamma(\theta) = 2e^{-jN\theta} \left[\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots + \frac{1}{2} \Gamma_{(N-1)/2} \cos \theta \right]$$

For N odd

Finite Fourier Cosine Series

By choosing the Γ_{ns} and enough sections (N) we can achieve the required response.

Binomial Multisection
Matching Transformers

Chebyshev Multisection
Matching Transformers