

Inductive Adders

Pulsed Power Engineering
Michigan State University
February 3 – 7, 2025

Craig Burkhart and (Guest lecturer) Tony Beukers



SLAC National Accelerator Laboratory

Will Waldron



Lawrence Berkeley National Laboratory

Chris Jensen



Fermi National Accelerator Laboratory

Jared Walden and (Guest lecturer) G. Chris Pappas (retired)



Oak Ridge National Laboratory





Course Outline

- Linear induction accelerators and inductive adders
- Impedance and propagation of adder structure
- Adder advantages/disadvantages
- Core considerations
- Examples of adders
- Minimizing rise time of adders
- Adder design example




Linear Induction Cavity

- An external voltage as shown in (a) is used to accelerate charged particles due to Lorentz force. Adding another accelerating structure to the right would require isolation of the voltage source.
- A cavity is created in (b), which is convenient for keeping the power supply at ground, but allows for high currents.
- A core is added to the cavity in (c) to create a large impedance to ground for high frequency or pulsed voltages to limit ground current.

  


*[1]

Linear Induction Accelerator

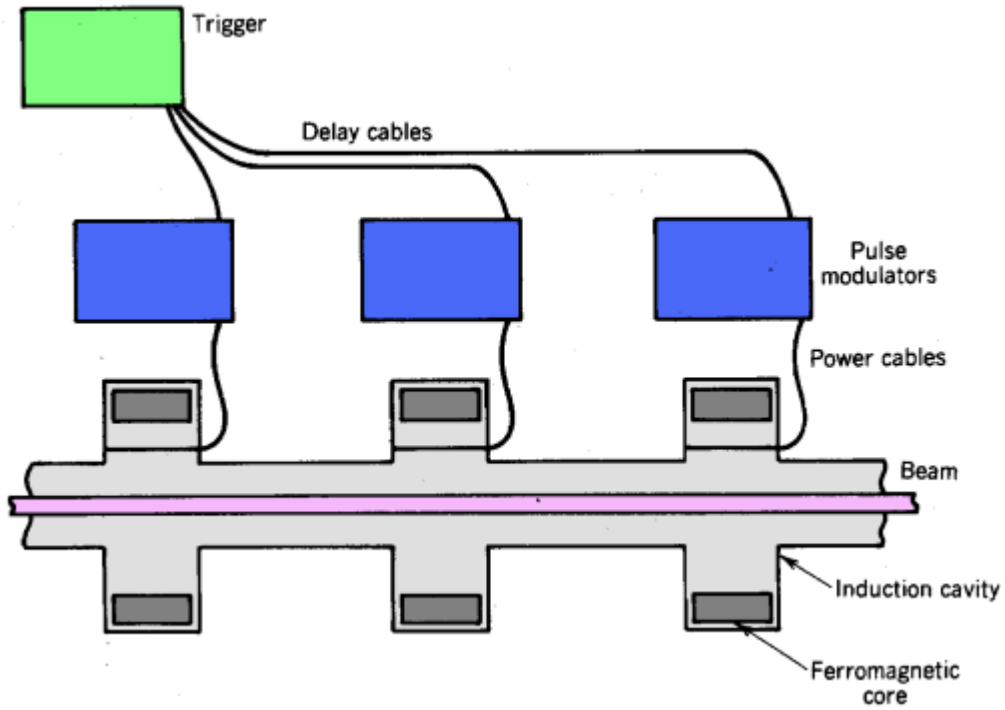

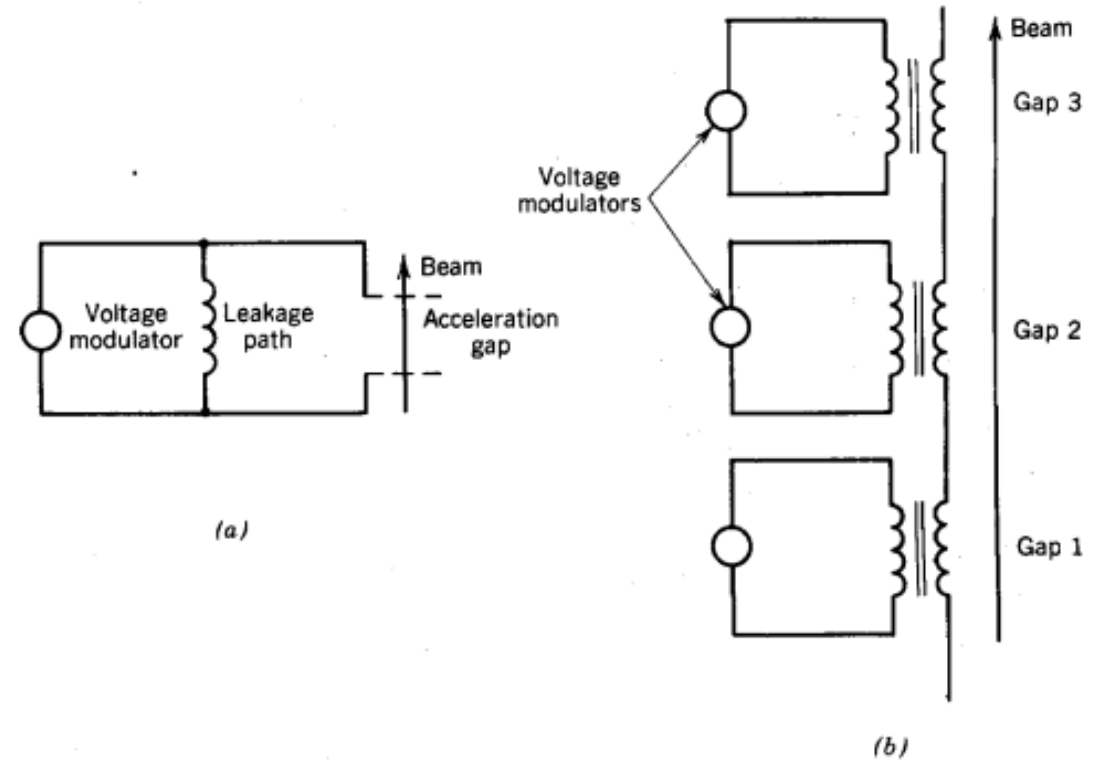Three induction cells in a linear accelerator.




Equivalent circuit of a 3 cell induction linac.

*[1]

Solid State Inductive Adder

- Analogous to an induction linac but using a wire to pass through the cores to form a secondary winding of a transformer.
- N identical low (limited by switch) voltage modules
 - Hard tube
 - MOSFET
 - IGBT
 - Linear amplifier
- Each module drives a single-turn high bandwidth output transformer
- The transformer secondaries are connected in series to inductively add the voltage of the individual modules
- Modules remain at ground potential throughout the pulse

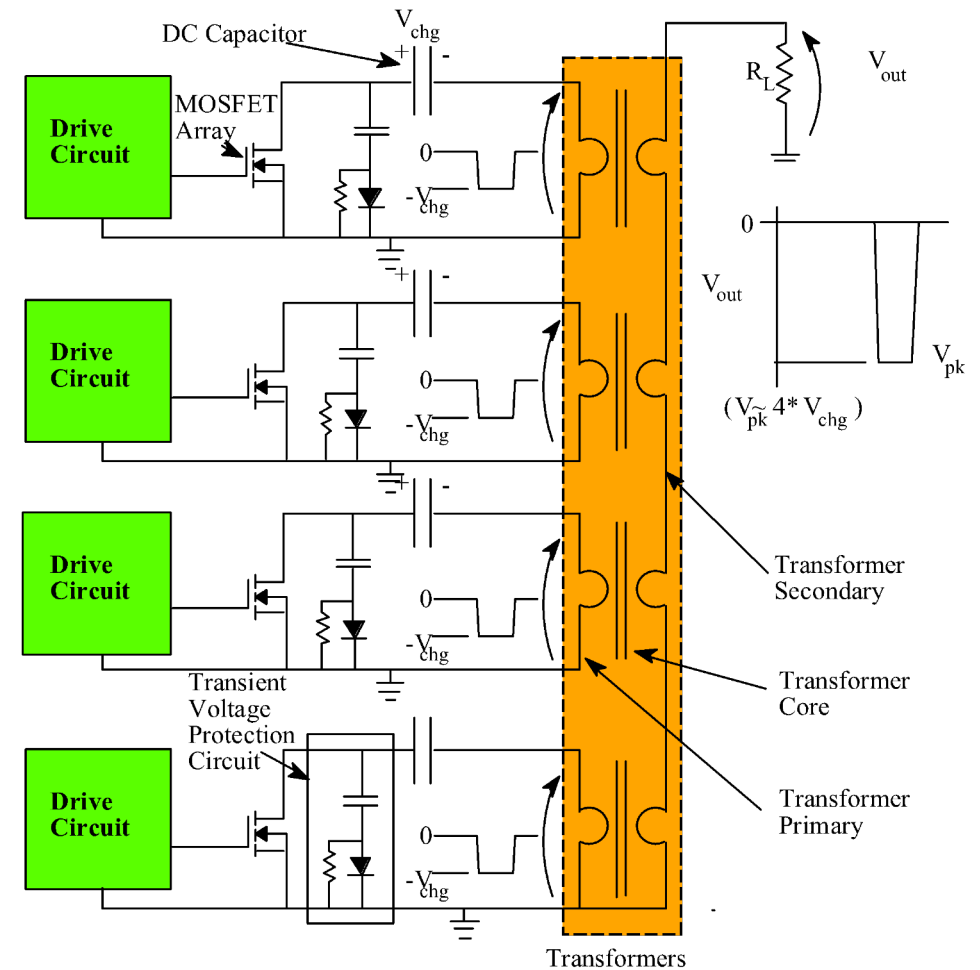

Impedance of Adder


- The impedance of the structure can be calculated as:

$$Z_a = \sqrt{\frac{L_p + L_a}{C_a}}$$

$$L_a = \frac{\mu h}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$C_a = \frac{2\pi\epsilon h}{\ln\left(\frac{b}{a}\right)}$$

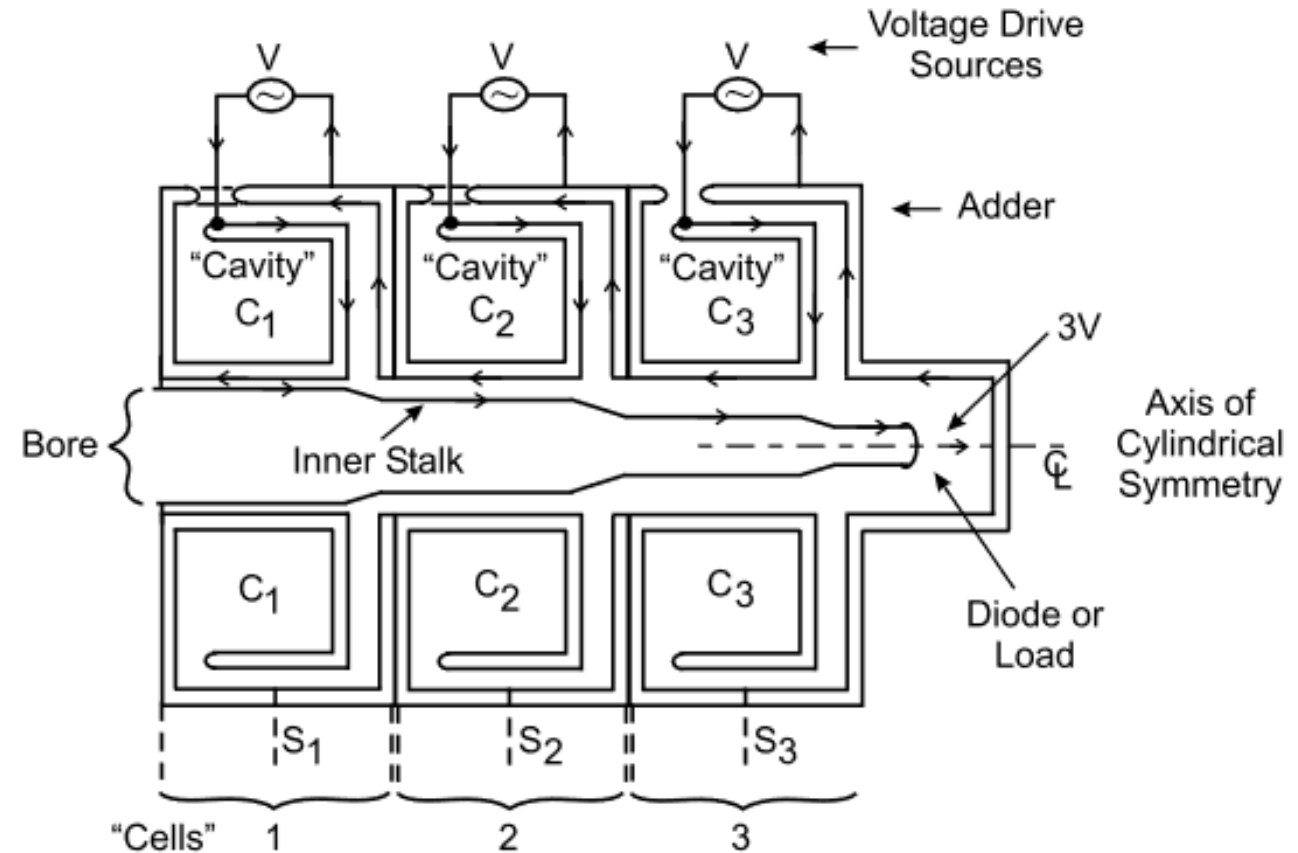L_p is the primary inductance, h is the height of a cell, b is inner diameter of core housing and a is outer diameter of the secondary.




*[2]

Propagation Time of Adder

- The propagation time for the structure is calculated by:

$$\tau \approx 2N \sqrt{L_p \frac{2\pi\epsilon h}{\ln\left(\frac{b}{a}\right)} + h^2\mu\epsilon}$$

 The propagation time is dominated by the height of the adder structure. For fast rise time, use as short a cell height as possible to support the volt-seconds and droop requirement, a low value of dielectric constant, and minimize the primary inductance.



Inductive Adder Topology - Advantages

- All drive components ground referenced
- No high voltage grading required (except transformer secondary)
- Pulse format defined by programmable pulse generator
 - Pulse width agility
 - Burst frequency agility
 - High burst frequency >1 MHz
- Modular - adder consists of stack of identical modules
 - All modules switch same voltage/current
 - All modules triggered simultaneously
 - Scalable to higher voltages by adding modules
- Low source impedance
 - Can drive wide range of load impedances
 - Load voltage is essentially independent of load



Inductive Adder Topology - Issues

- Each module must switch full load current
 - May require many parallel components (switches, capacitors, etc.)
 - Parallel switching devices must have low jitter on both turn-on and turn-off
- Requires very low inductance in primary circuit
- Requires very fast opening switch that can interrupt full load current and survive fault currents
- Fault currents can be very large, especially if cores saturate
- Cost
- Complexity



Inductive Adder Design Considerations

- Select Switch and switch drive circuit
 - Switching speed for both turn-on and turn-off
 - Maximum operating voltage (determines number of modules)
 - Current Rating (determines number of parallel devices)
- Size the capacitor (bank)
 - Must be large enough to meet droop requirements
 - Inductance must be low
 - Low ESR (equivalent series resistance)
- Design the pulse transformer
 - Use high frequency core material
 - Core area must be sufficient for application
 - Total volt-seconds for single pulse if reset between pulses
 - Total volt-seconds for all pulses in burst if reset between bursts



Inductive Adder Design Considerations



- Make sure that primary circuit inductance is minimized
 - Voltage drop across loop inductance during high di/dt affects load voltage
 - Energy stored in loop inductance can appear as voltage across switch
 - Consider component inductances, transformer leakage inductance, and inductance of circuit board traces
- Protection circuits for switches
 - Overvoltage from $(L di/dt)_{\text{primary}}$ on turn off
 - Overcurrent; load faults, transformer saturation
- Reset of adder magnetic core
 - Duty cycle sets minimum ratio for $V_{\text{reset}}/V_{\text{output}}$ (total $V\tau = 0$)
- Recharge of capacitor between pulses/bursts
 - Interpulse recharge can reset core if voltage and current high enough




Magnet Core Hysteresis

- For ferromagnetic materials, the relative permeability μ_r is not linear, $\mathbf{B} = \mu_r \mu_0 \mathbf{H}$.
- Relative permeability varies with magnetic field, frequency and temperature and reaches saturation where the magnetization of the core does not increase further with applied field, ~15 kG for the core at right.
- You may see it plotted as volt-seconds vs Ampere.

*[2]

 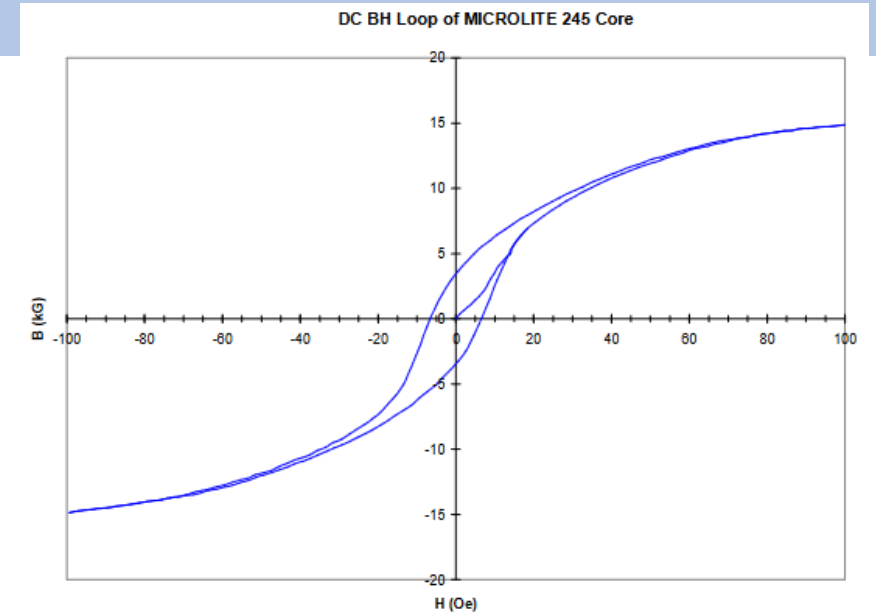


Relative Permeability

 

*[3]

Complex Permeability vs. Frequency

 


*[4]



- Relative permeability drops with increasing frequencies and is a function of the core material used.
- Iron based cores generally have higher initial permeability than ferrite cores.
- Ferrite cores generally support higher frequencies before rolling off.

Core Loss

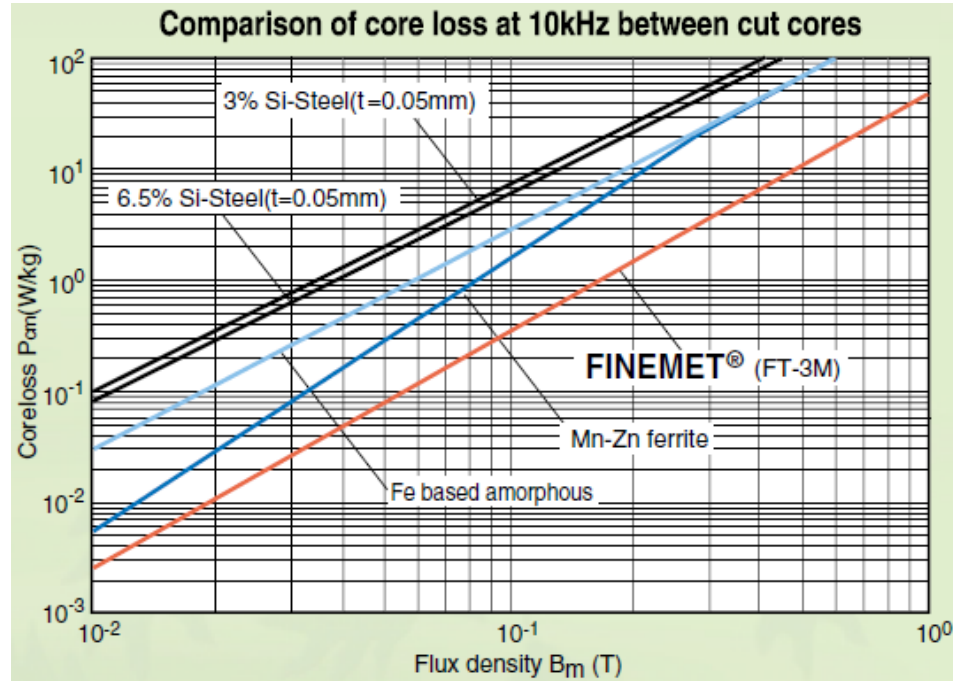- Core loss is given as W/kg, and is dependent on frequency, flux swing and temperature.
- All should be considered in the design of an adder, especially at high pulse rates.




*[3]

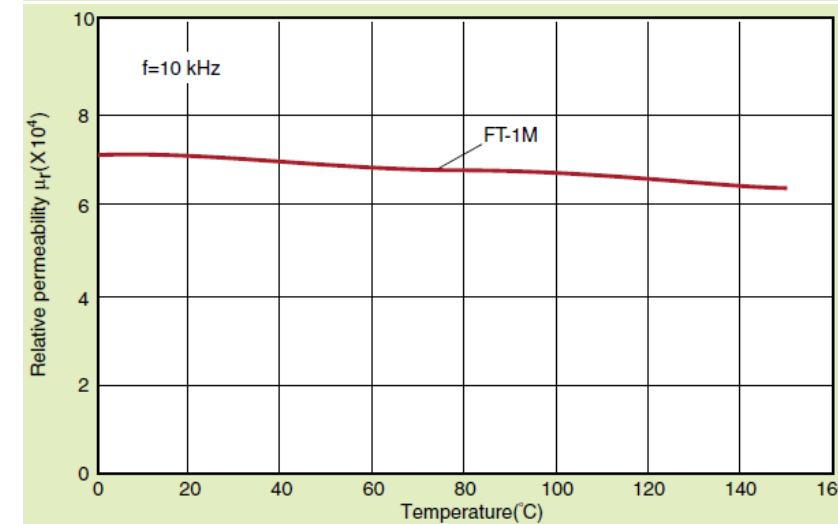 

Core Reset/Bias Circuit

- Voltage induced into the primary resets the magnetic core material between bursts
- H-field created by the DC current biases the magnetic cores to a single point on the BH curve.
- Reset through the secondary winding resets all the cores
- The series inductor protects and isolates the reset power supply from the high voltage output pulse
- Other reset circuits can be used: DC reset through the primary, pulsed current into either the primary or secondary

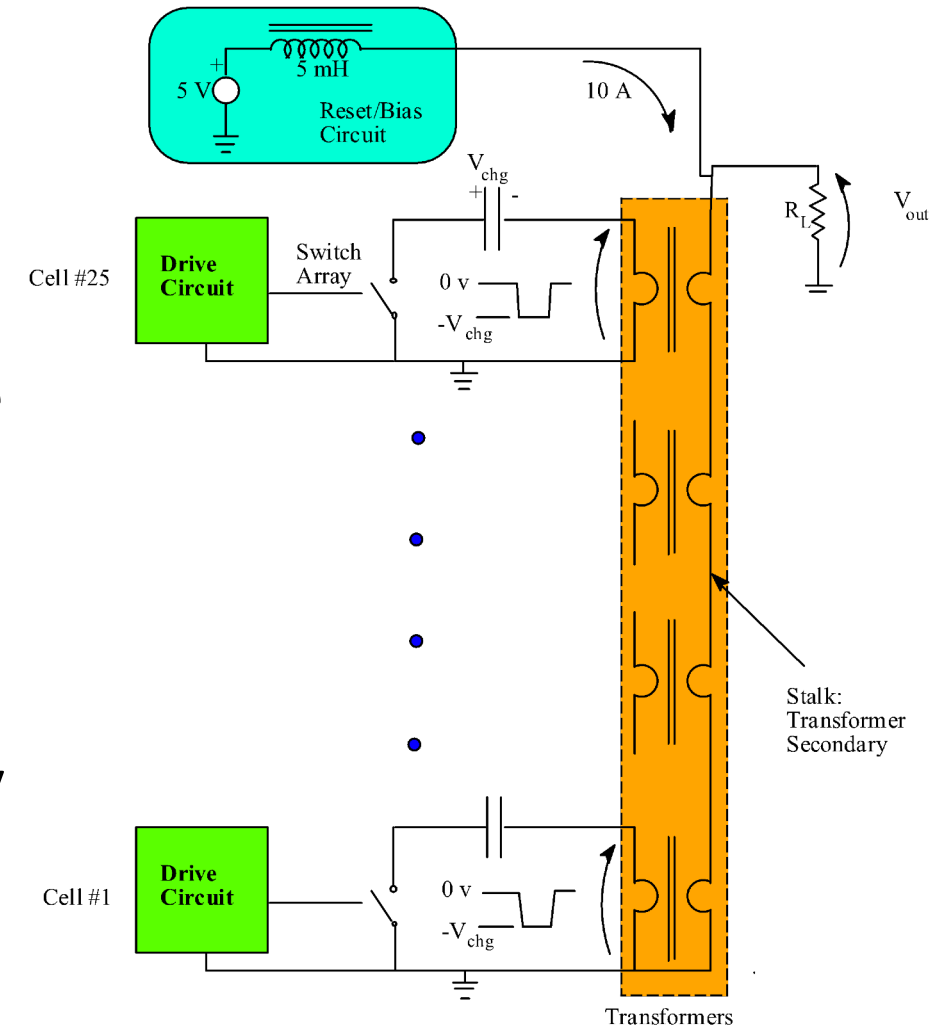


Core Magnetizing Inductance



An inductive voltage spike at the end of the pulse can damage the switch.

Adding a freewheel diode across the primary protects the switch, but allows magnetizing current to circulate in the primary.

 You may need to add a resistor in series with the diode for fast turn off.



Short Circuit Protection

 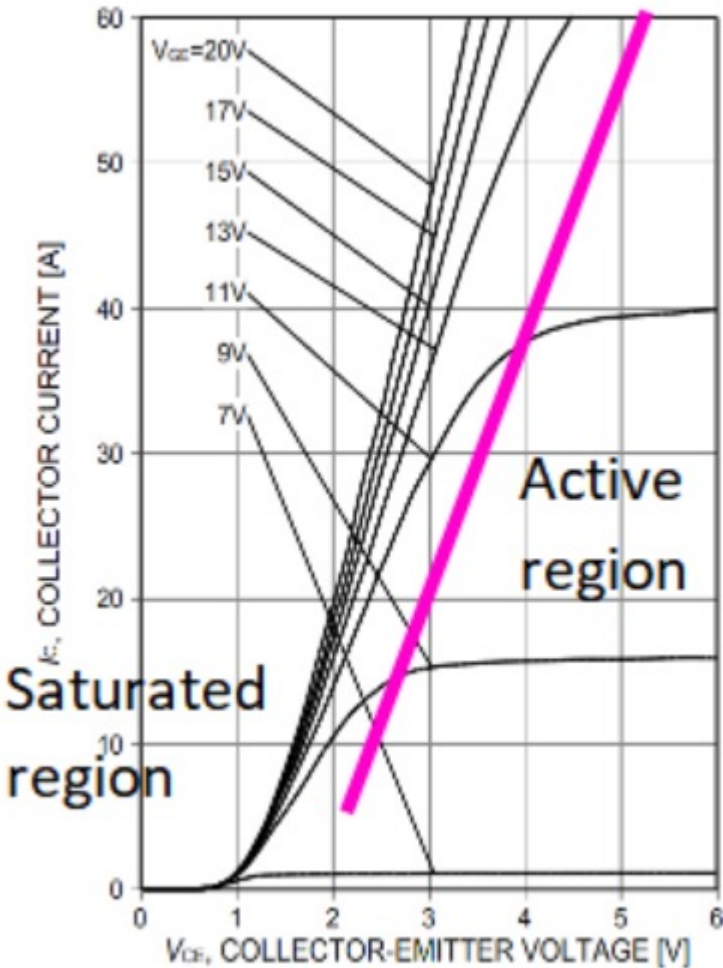

IGBTs operating in the active region have high losses. For pulses $> 1 \mu s$ long, you need to protect the switch from short circuits at the load. Core saturation is particularly damaging. Use a de-saturation protection circuit and drive the IGBT at the lowest voltage possible to meet the current and rise times requirements.

Example 1 - NLC Solid-State Modulator

- Why use inductive adder
 - 2 TeV center of mass collider using 2000 klystrons, for comparison SLC was 100 GeV center of mass with 200 klystrons and operated at about 50 MW average power.
 - Would need a dedicated power plant to provide power and a maintenance crew of 100s based on SLAC experience and scaling.
 - SS inductive adders offered improvements in cost, efficiency and maintainability over PFN/thyratron modulators.
- Modulator Requirements:
 - Output Voltage 500kV @ 2kA
 - Pulse-width - 3 μ s
 - Klystron Efficiency > 80% (rise & fall times less than 400 ns)
 - Repetition Rate - 120 Hz (500kW Average)
 - Lifetime - 30 years
 - Cost < 200k\$/ Modulator
 - Each modulator drives 8 klystrons





Example 1 - NLC Modulator


- FRACTIONAL TURN PULSE TRANSFORMER
 - MULTIPLE PRIMARIES ONE END GROUNDED
 - 76 Primaries with 3 turn Secondary
 - Primary uses low losses Metglas (or Finemet) cores
 - SECONDARY CONNECTED IN SERIES
 - 500 kV @ 2080 A, 1040 Meg watts for 4 μ s at 120 Hz, 500 kW Average uses solid-state IGBT driver
 - **IGBTs** ARE BIPOLAR TRANSISTOR WITH FET INPUT GATE
 - 152 IGBT's (two per Primary)
 - 3200 Amps, 4 μ s pulses each IGBT
 - 2200 volts per IGBT rated at 3.3 kV-800 A
- MAJOR CONCERNS
 - Klystron protection when there are internal faults (limit energy in klystron arcs)
 - IGBT protection when load faults (requires active sense and control circuitry)



NLC - IGBT Drivers and Core

  

 
First prototype used two parallel, 3.3 kV IGBTs driving a METGLAS core. The cores were reset between pulses. A freewheeling diode is used to bypass cells allowing rise time/flat top shaping.



Prototype NLC Solid State Induction Modulator




 
3 turn Secondary with 3 S-band klystrons and a water load installed





With HV oil tank installed

Prototype NLC Secondary Structure

  Coaxial Nested Three Turn Secondary End Connection




Klystron heater cables

  


Output connector to 8 klystrons

Prototype NLC Modulator - Water Load

 Three Turn Secondary
76 Metglas cores
152 IGBT Drivers




 NLC Adder Cell w/Drive Boards (with 6.5kV IGBTs)




Comparison: Voltage Pulse of Induction Modulator vs. PFN

350 kV, 3.0 usec
375 Amps PFN
750 amps Induction
Modulator waveform
efficiency ~89%
Overall efficiency >80%

 

Example 2 – Darht-2 Kicker Modulator

Parameter	Requirement
Output Voltage	$\pm 20\text{kV}$ into 50Ω
Voltage Rise/Falltime	$\leq 10\text{ns}$ (10-90%)
Flattop Pulsewidth	16ns–200ns (continuously adjustable)
Burst Rate	4 pulses @1.6MHz (~600ns between leading edges)

 


*[5]




Bi-polar Induction Adders

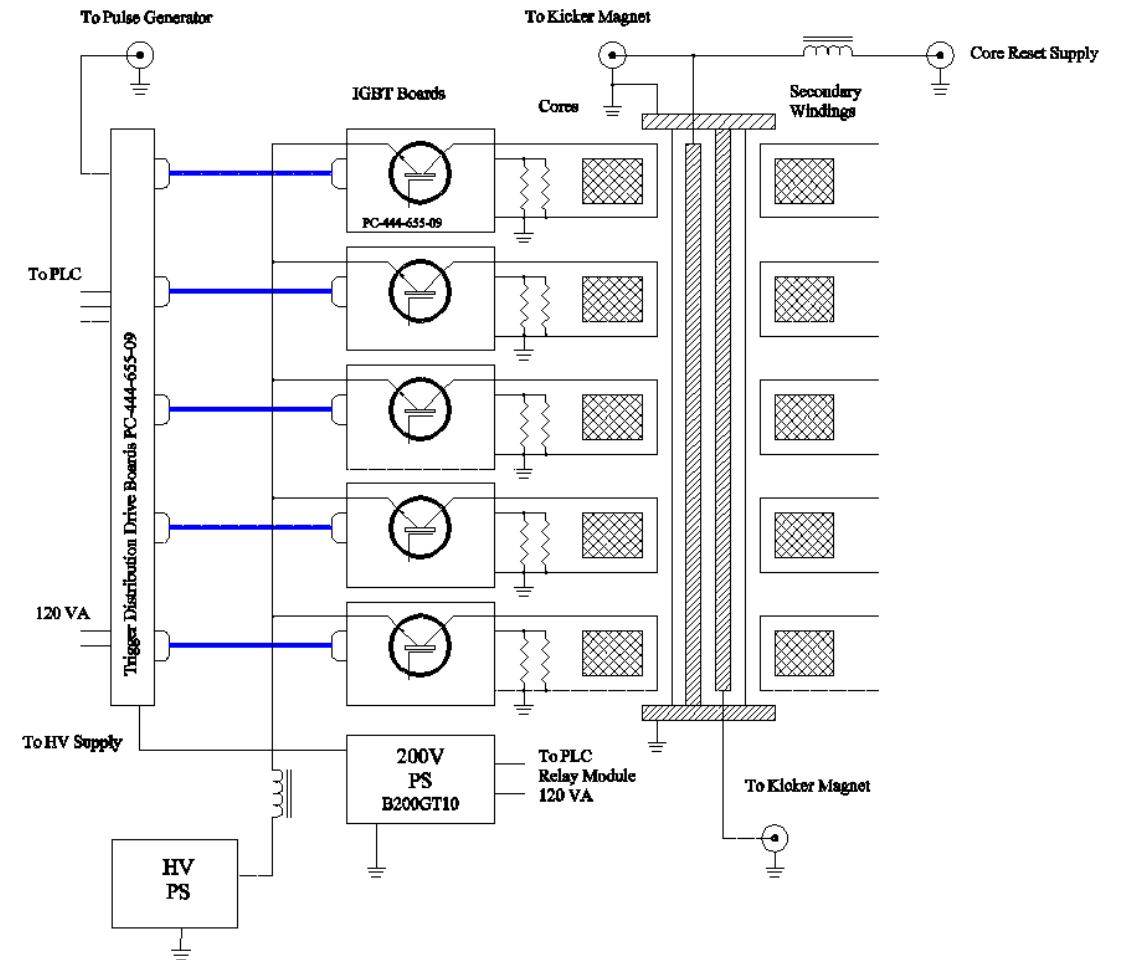- Using two secondaries wound in opposite directions make for a bi-polar adder as shown.
- Five cells, each with a single turn primary and bi-polar single turn secondaries.
- Pulses are nearly identical.
- Good choice for driving pulsed magnets (stripline).




Spear 3 Kicker Modulator

 - ± 10 kV and ± 20 kV, depending on magnet
- 2620A and 2380 A, depending on magnet
- Five and ten cells, depending on magnet
- 375 ns rise time/fall time
- 750 ns pulse width




10 cell adder

5 cell adder

 


ALS-U Kicker Modulator

 - Eight cell bipolar adder
- $V_o = \pm 5300 \text{ V}$ into 50Ω
- Rise fall times $< 10 \text{ ns}$.
- Uses 16 parallel MOSFETs per cell.
- Adder structure is designed to be 25Ω .
- Triggering can be adjusted for each MOSFET to compensate for variations in gate capacitance and optimize rise time.



Commercial Inductive Adder Modulator

 - 20 kV
- 100A
- 100 ns pulse, ~15 ns rise/fall
- To 25 kHz
- To 3 kW




Other Commercial Suppliers

- Scandinova, Sweden
- Ampegon, Switzerland
- Jema, Spain
- Diversified Technologies, USA
- Others




Reflections in the Structure

- Consider the structure shown, assuming $R_l = Z_0$ and only C_3 is driven. Diodes in C_1 and C_2 turn on, bypassing those cells and $V_o = V$.
- A wave propagates with an impedance of $Z_0 / 2$ from C_3 to both the right and left, reflecting off a short on the left and R_l at the right.
- Wave continue to reflect, until damped by the load, effectively adding several propagation delays to the rise time.

 

Minimizing Reflections

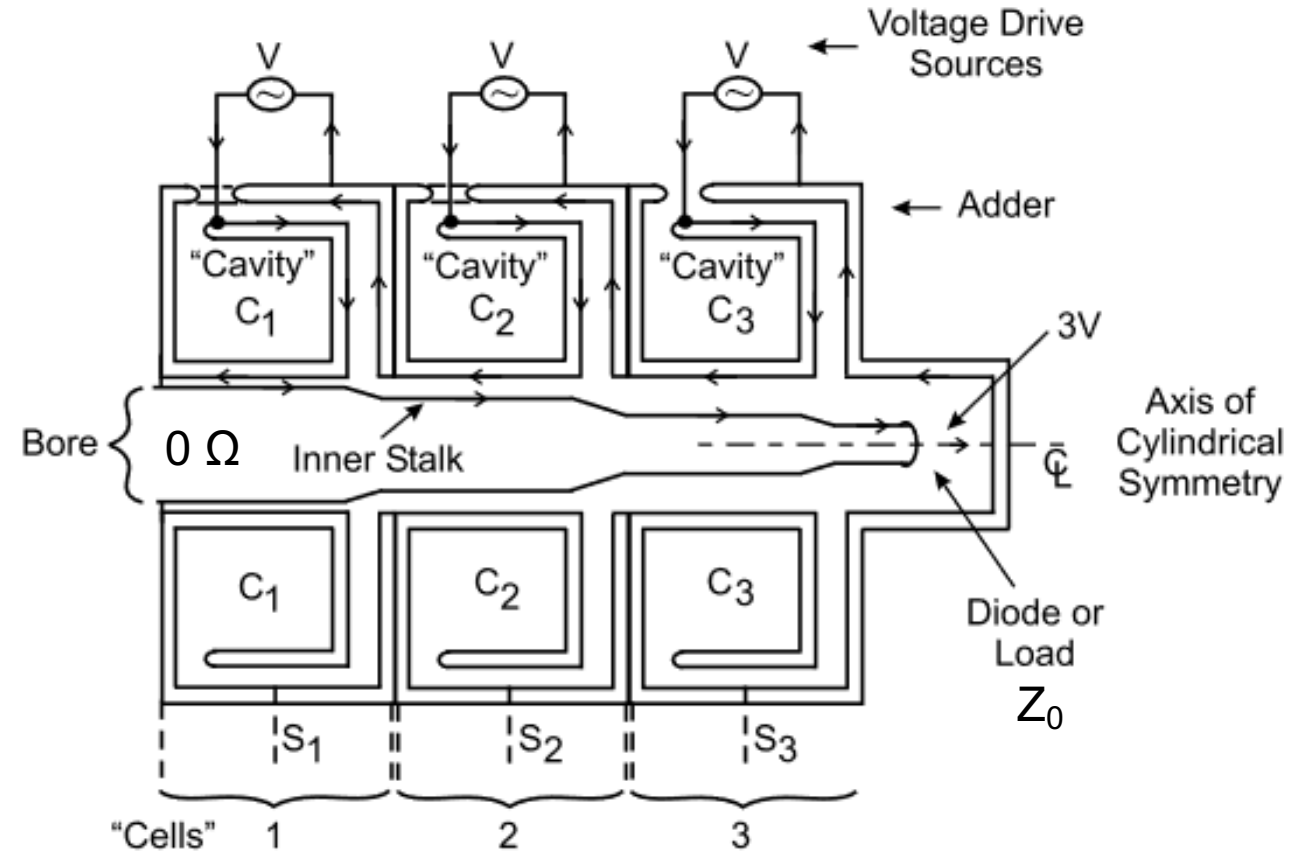- Tapering the adder secondary structure from Z_0 at the load end to 0Ω at the shorted end will reduce the reflections and increase the rise time.
- Difficult to build tapers for bipolar adders.




Delayed Triggering

- Delaying trigger of a cell to match the transmission to from the shorted end will minimize the rise time of the pulser.
- Trigger source for C1 first. At trigger C2.

$$t = \sqrt{L_p \frac{2\pi\epsilon h}{\ln\left(\frac{b}{a}\right)}}$$

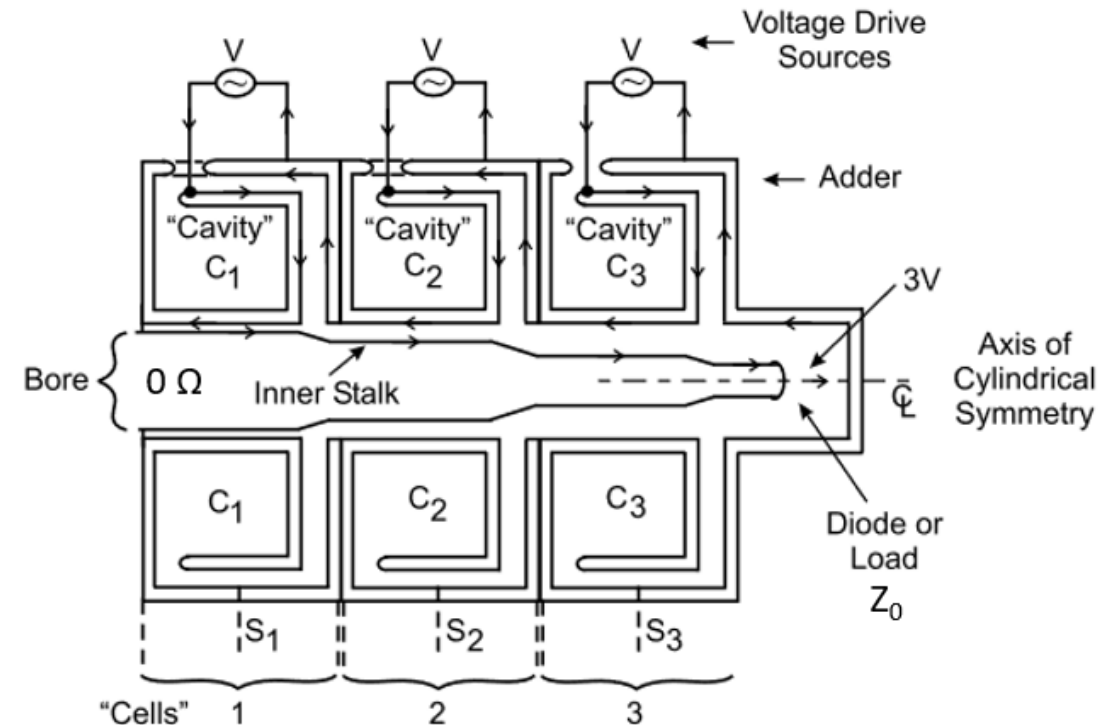- Trigger C3 delayed from C2 by the same amount.
- All wavefront arrive at the load at the same time.
- Only works for unipolar adder.



Design Example

- We have decided to use a solid state inductive adder to drive S-band klystrons with peak cathode voltages of 320 kV and peak current of 350 A. Pulses are 3 μ s at 100 Hz with rise and fall times of less than 500 ns. Flat top requirement is $\pm 1\%$ full scale.
- We need to:
 - Select which switches to use.
 - Determine how many cells are needed.
 - Select core material and design the cells for the adder.
 - Size and select the pulse capacitors.
- Is a step-up transformer needed? What should the turns ratio be?
- What rise time can you expect from the modulator?



Example: Switch Selection & Number of Cores

- Since peak and average power levels are fairly high, and the rise and fall times are moderate, a good choice for this design is to use IGBTs for switches.
- Would like to use highest power IGBTs available since that reduces the number of cells required. Could run into other constraints such as core size and cost.
- I chose Infineon FZ1200R45HL3_S7, 4.5 kV, 1200 A devices for this design to keep the number of cells and cores sizes moderate.
- For the 4.5 kV device I chose a maximum V_{CE} of 3200 V and a maximum I_E of 3200 A.



Example: Number of Adder Cells and Turns Ratio

- Adder output voltages and IGBT currents are shown below for various number of cells and secondary turns ratio.
- Voltage is calculated by VCE chosen times number of cells times turns ratio.
- IGBT current is calculated from the tube perveance at the calculated output voltage

Number of Cells	Vo with 5:1 Secondary	Vo with 6:1 Secondary	Vo with 7:1 Secondary	Vo with 8:1 Secondary	Ie with 5:1 Secondary	Ie with 6:1 Secondary	Ie with 7:1 Secondary	Ie with 8:1 Secondary
8	128000	153600	179200	204800	4.43E+02	6.98E+02	1.03E+03	1.43E+03
10	160000	192000	224000	256000	6.19E+02	9.76E+02	1.43E+03	2.00E+03
12	192000	230400	268800	307200	8.13E+02	1.28E+03	1.89E+03	2.63E+03
14	224000	268800	313600	358400	1.02E+03	1.62E+03	2.38E+03	3.32E+03
16	256000	307200	358400	409600	1.25E+03	1.98E+03	2.90E+03	4.05E+03
18	288000	345600	403200	460800	1.49E+03	2.36E+03	3.47E+03	4.84E+03
20	320000	384000	448000	512000	1.75E+03	2.76E+03	4.06E+03	5.67E+03

Chose 14 cell adder with 8:1 ratio.

Example: Core Selection & Size

- Core size is calculated from $Vs = N\Delta BA$, where V is the switch voltage, s is the pulse width, N is the number of primary turns, ΔB is the flux swing in the core and A is the cross sectional area of the core.
- Since the rise and fall times are relatively slow, I can use an iron based core material with thin laminations.
- For low core loss, I selected a tape wound Metglas 2605 SA1 material with a saturation flux of 1.56 T and assumed a stacking factor of 0.8. I assumed the core will be reset between pulses. For 1" ribbons I end up with a core cross section of 1" X 7.95".
- The magnetizing inductance contributes to droop and be calculated for a cell by $L_m = \mu A / l_m$ where μ is permeability of the core material A is the cross sectional area and l_m is the mean magnetic length.

Example: Capacitor Selection

- Neglecting the magnetizing inductance, we want less than 64 V (2 %) droop from the capacitor for 3200 A, 3 μ s pulses, so the capacitor should be $> 155 \mu\text{F}$.
- We want capacitors with low ESR due to the peak currents which leads us to plastic film capacitors for such a large value. This is a good choice since they are stable and have low voltage coefficients.
- Available from a variety of manufacturers with a range of form factors.



Inductive Adder Example 2

Say we wanted to drive two klystrons with a single inductive adder:

Beam voltage, 420 kV

μ Perveance, 1.2 each

Pulse Width, 1.5 μ s

PRF, 120 Hz

Using a two 6.5kV, 750 A switch per cell and an output transformer, how many cells should be used and what is the output transformer turns ratio?



Example 2

Switch selection – Infineon DD750S65K3, 6500 V, 750 A rated. Operate at 4000 V and 3000 A peak.

Equivalent perveance is $2.4 \text{ e}^{-6} \text{ A/V}^{3/2} \Rightarrow I_{\text{peak}}=653 \text{ A}$. Maximum turn ratio of transformer is $6000 \text{ A}/653 \text{ A}=9$. Therefore, the peak voltage from the adder is 47 kV.

For a 47 kV adder using switches operating at 4 kV, you need 12 cells.

References

- [1]. Humphries, S., Principles of Charged Particle Accelerators, 1999.
- [2]. Smith, I.D., Induction voltage adders and the induction accelerator family, Physics Review Special Topics - Accelerators and Beams, Vol. 7, 2004.
- [2]. Hitachi Metals, 2605SA1 data sheet.
- [3]. Hitachi Metals, Finemet FT3 data sheet.
- [4]. Ceramic Magnetics, Inc., CMD5005 data sheet.
- [5]. Cook, E.G., et al, Inductive-Adder Kicker Modulator for Dahrt-2, 20th International Linac Conference, Aug. 2000.

